

**Roll No: 20P-0101**

**Name: Muhammad Sherjeel Akhtar**

**Section: BCS-2D**

**Assignment NO: DLD LAB ASSIGNMENT 10**

**Submitted To Respected Maam: Anam**

## Lab 10

### To Design and Implement Multiplexer & Demultiplexer


**Note: For all the circuits in the tasks, your logic diagrams should be either hand drawn or from the software logicly. Keep them neat and legible. These circuits will be having many connections so, for simulations, make sure that you label the inputs and outputs clearly. Use Label tag in “logically”. You can also edit the pictures of your outputs in “paint” easily.**

#### Tasks

- 1. Construct a logic circuit for 8 to 1 multiplexer with the help of truth table. Also write the Boolean expression for output(s). Simulate your circuit to verify the outputs.**

#### 8 to 1 Mux

a) Block Diagram

 


b) Truth Table

b) Truth Table

$S_2$	$S_1$	$S_0$	$Y$
0	0	0	$D_0$
0	0	1	$D_1$
0	1	0	$D_2$
0	1	1	$D_3$
1	0	0	$D_4$
1	0	1	$D_5$
1	1	0	$D_6$
1	1	1	$D_7$
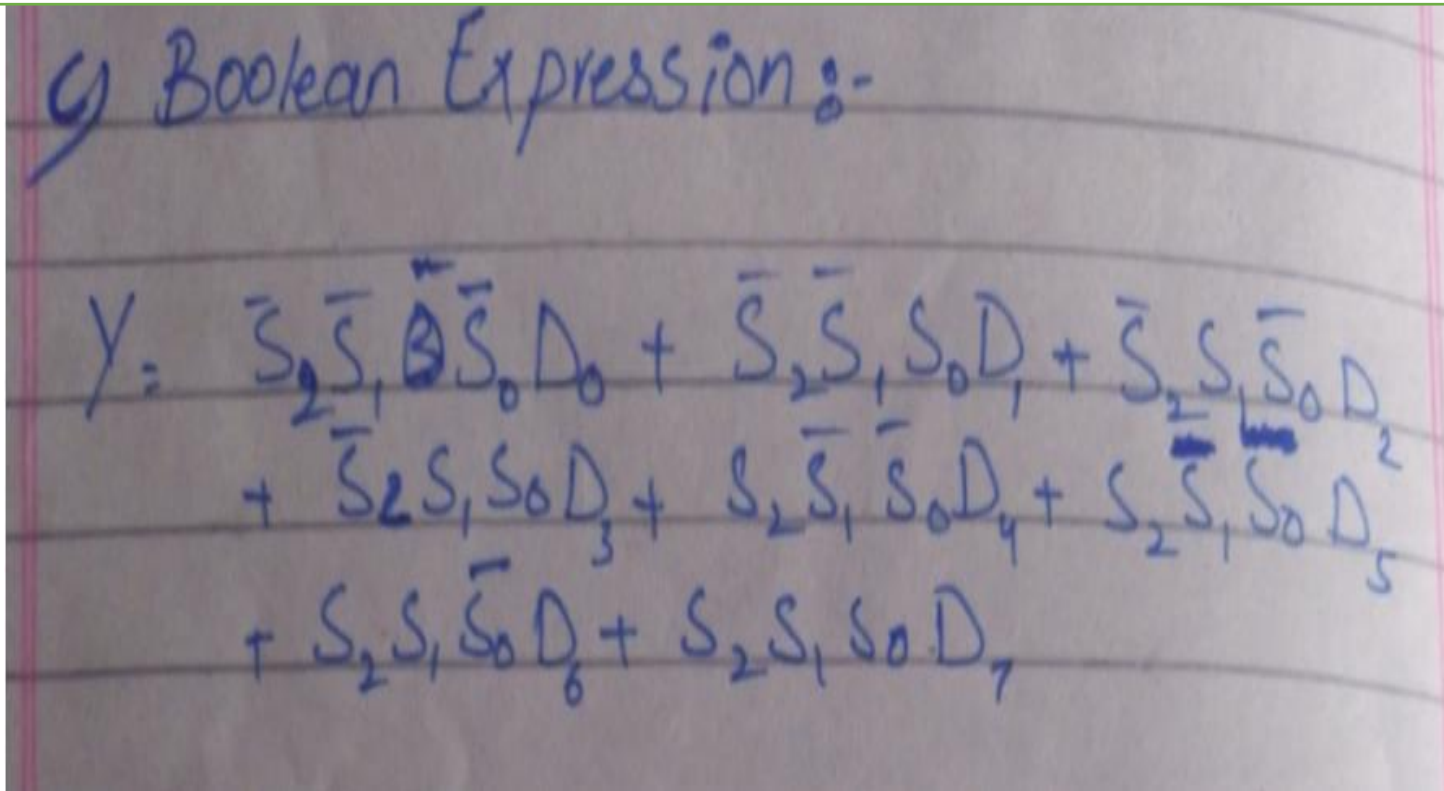
### c) Boolean Expression

20P-0101, Muhammad Sherjeel Akhtar, BCS-2D




g) Boolean Expression:-

$$Y = \bar{S}_2 \bar{S}_1 \bar{S}_0 D_0 + \bar{S}_2 \bar{S}_1 S_0 D_1 + \bar{S}_2 S_1 \bar{S}_0 D_2 + \bar{S}_2 S_1 S_0 D_3 + S_2 \bar{S}_1 \bar{S}_0 D_4 + S_2 \bar{S}_1 S_0 D_5 + S_2 S_1 \bar{S}_0 D_6 + S_2 S_1 S_0 D_7$$


d) Logic Diagram (from logically or hand drawn)

## Logic Diagram:

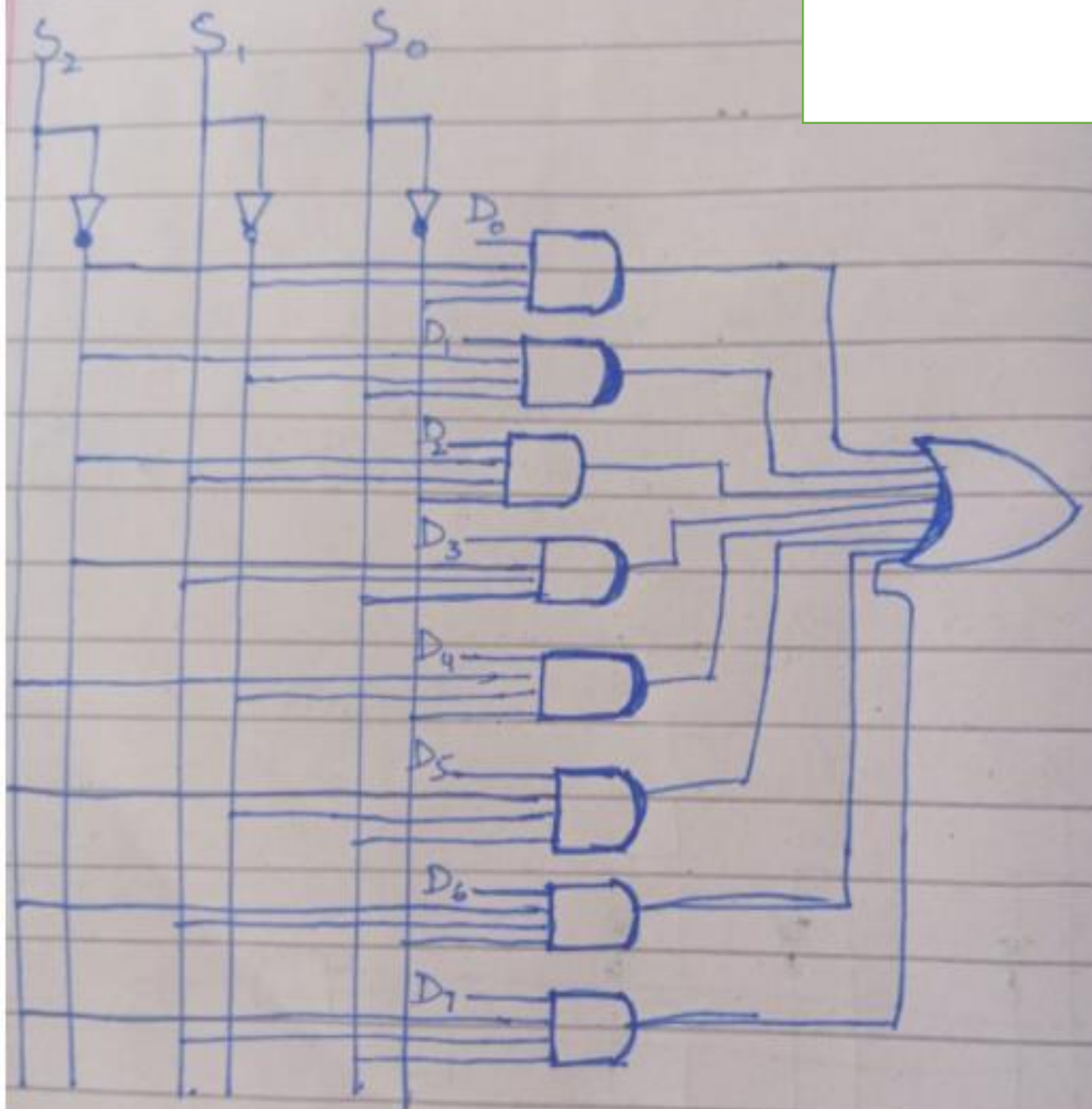
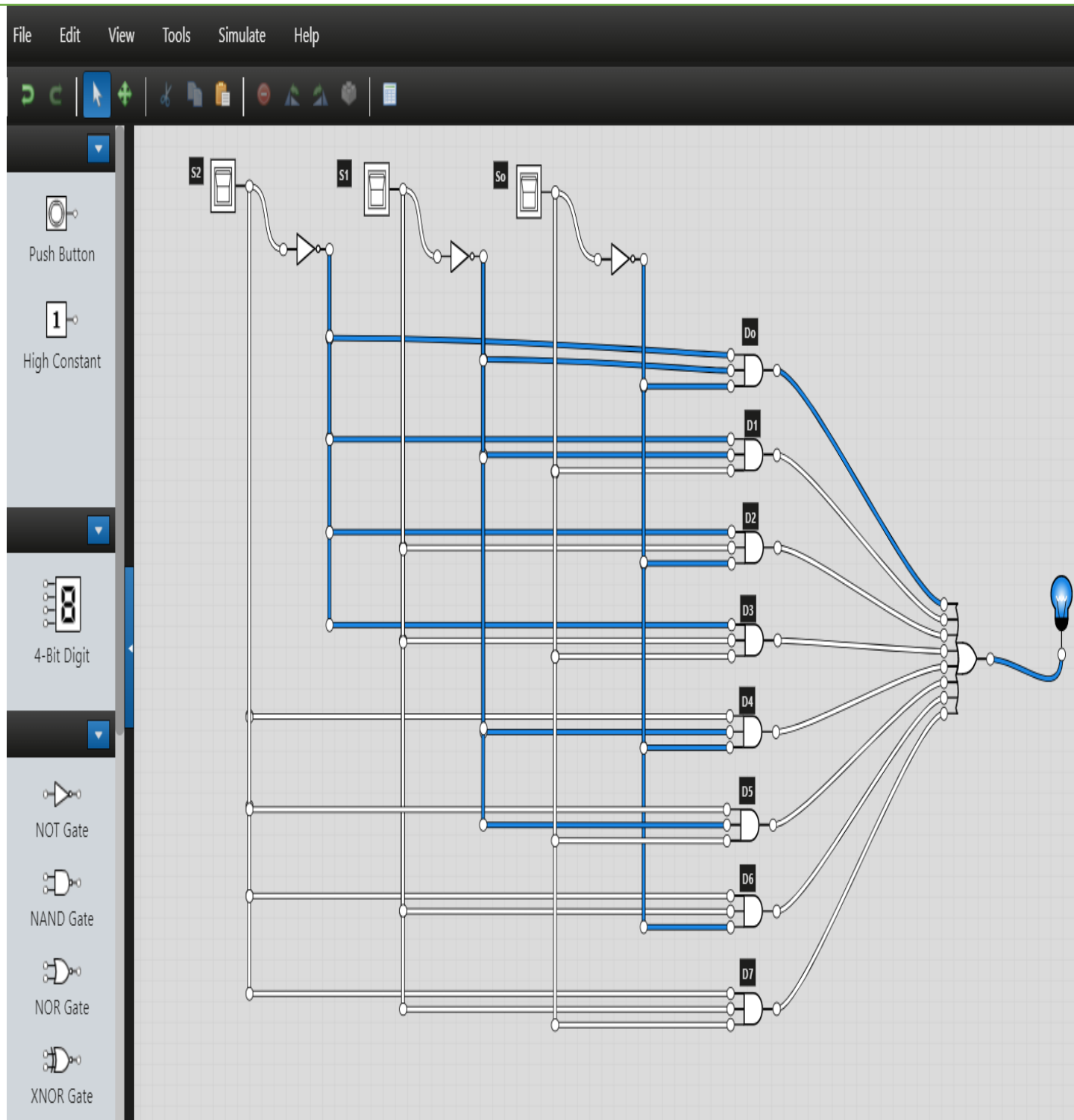
## e)Software Simulation

20P-0101, Muhammad Sherjeel Akhtar, BCS-2D



**2.Design a logic circuit for 1 to 4 line Demultiplexer. Also write the Boolean expression for output(s). Simulate your circuit to verify the outputs.**

**a)     Block Diagram, Truth Table, Boolean Expression**




Block Diagram :-Truth Table :-

$a$	$b$	D-output selected
0	0	A
0	1	B
1	0	C
1	1	D


Boolean Expression :-

$$F = \bar{a} \cdot \bar{b} A + \bar{a} \cdot b B + a \cdot \bar{b} C + a \cdot b D$$

## b) Logic Diagram

 


## c) Software Simulation

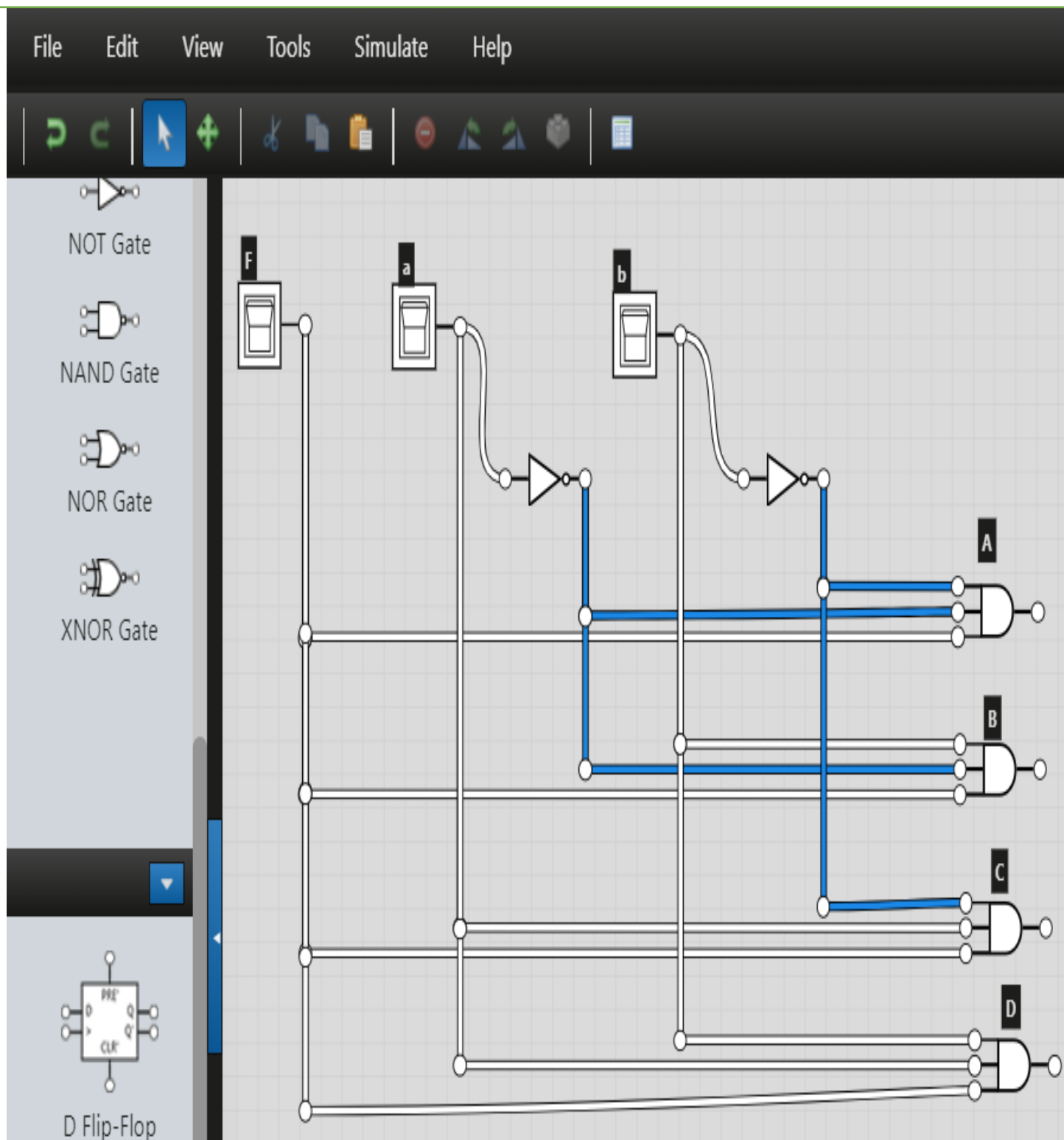

**3.Design a circuit for 4 to 1 Multiplexer using 2 to 1 Multiplexer(s). You can take help from google or the link below. Just ignore the coding language discussed in the link.**

*<https://bravelearn.com/design-of-4x2-multiplexer-using-2x1-mux-in-verilog/>*

**a)      Block Diagram, Truth Table**

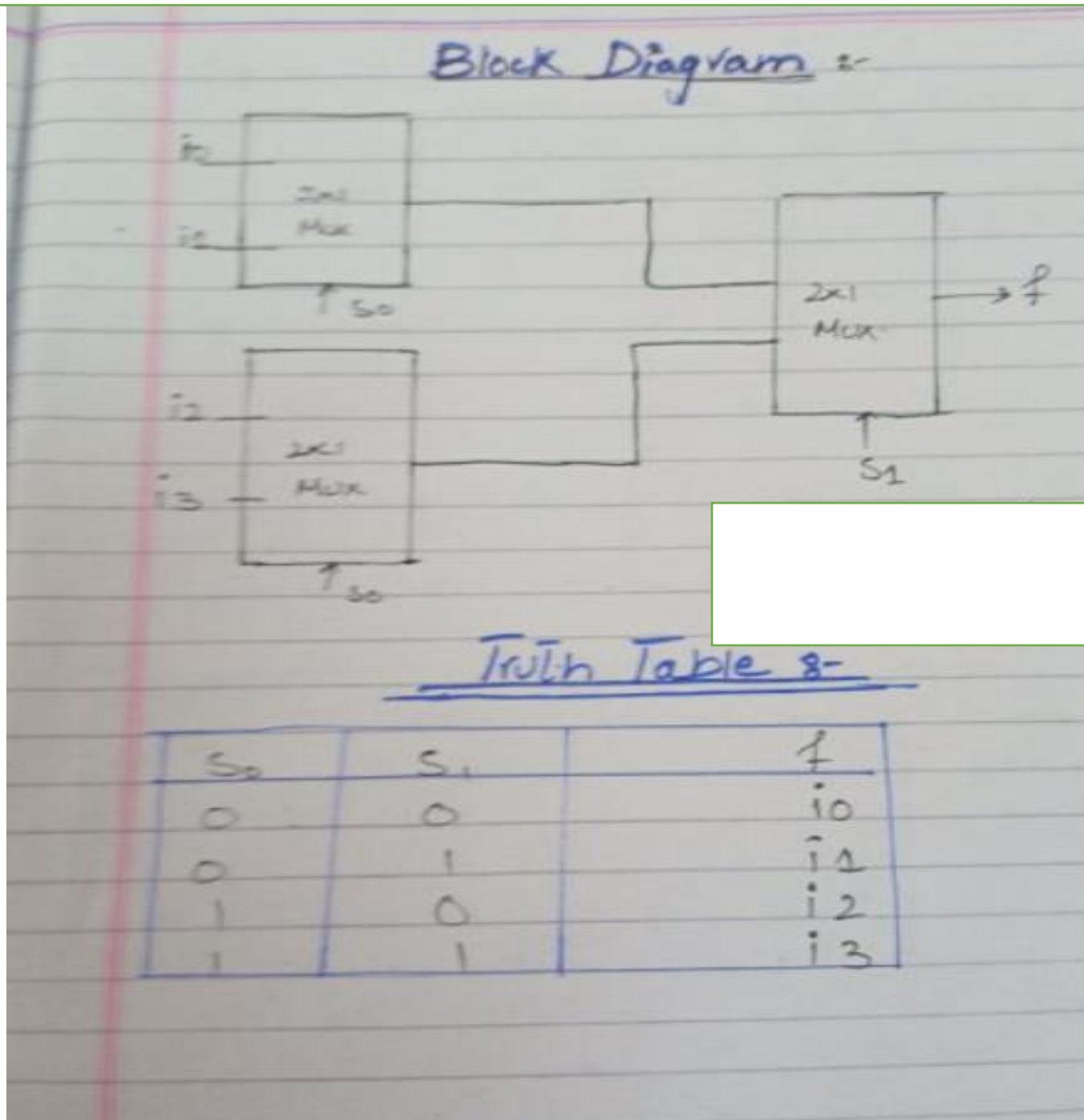

- b) Logic Circuit (on the basis of 2 to 1 Muxes used/follow the block diagram to draw this circuit)

*You need to connect three **2 x1 Multiplexers** in order to make one **4x1 Multiplexer**.*

## Logic Diagram:-

