

Name: Muhammad Sherjeel Akhtar

Roll No: 20P- 0101

BCS-2D1

Lab Task # 5

Lab 5

To Demonstrate the Working of Binary Adders

Note: You may draw all the logic diagrams with hand and paste the pictures here or on logicly software with your name, roll number & section mentioned in your workspace. Make sure that all of your connections are clearly visible and distinguishable.

Tasks

1. Construct a logic circuit for half and full adder with the help of truth table. Also write the Boolean expression for output(s).

Half Adder

a) Truth Table


A	B	SUM	COUT
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

b) Boolean Expression (Simplified)



SUM: $A \oplus B = A \text{ XOR } B$



CARRY: $A \cdot B = A \text{ AND } B$

c) Logic Diagram

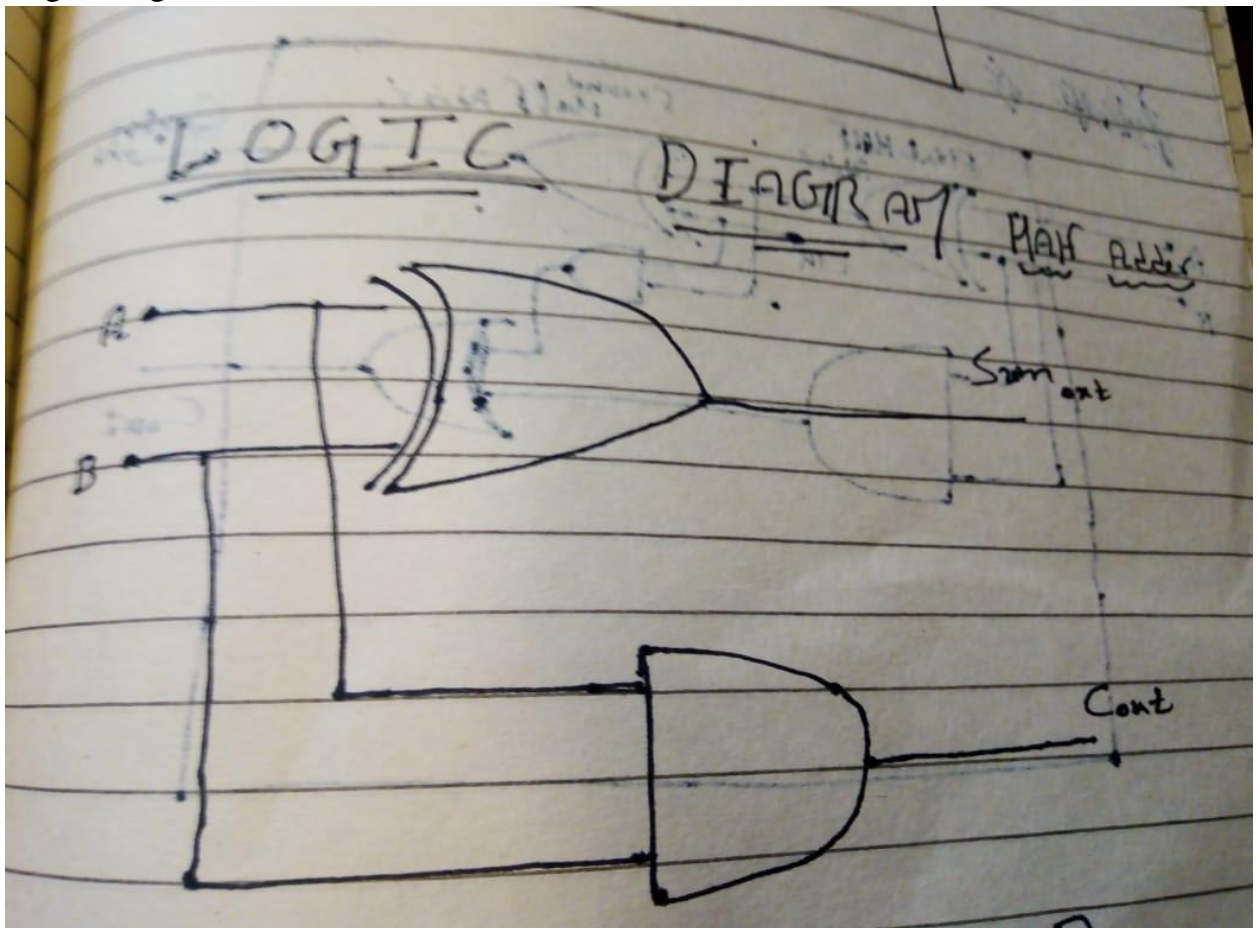

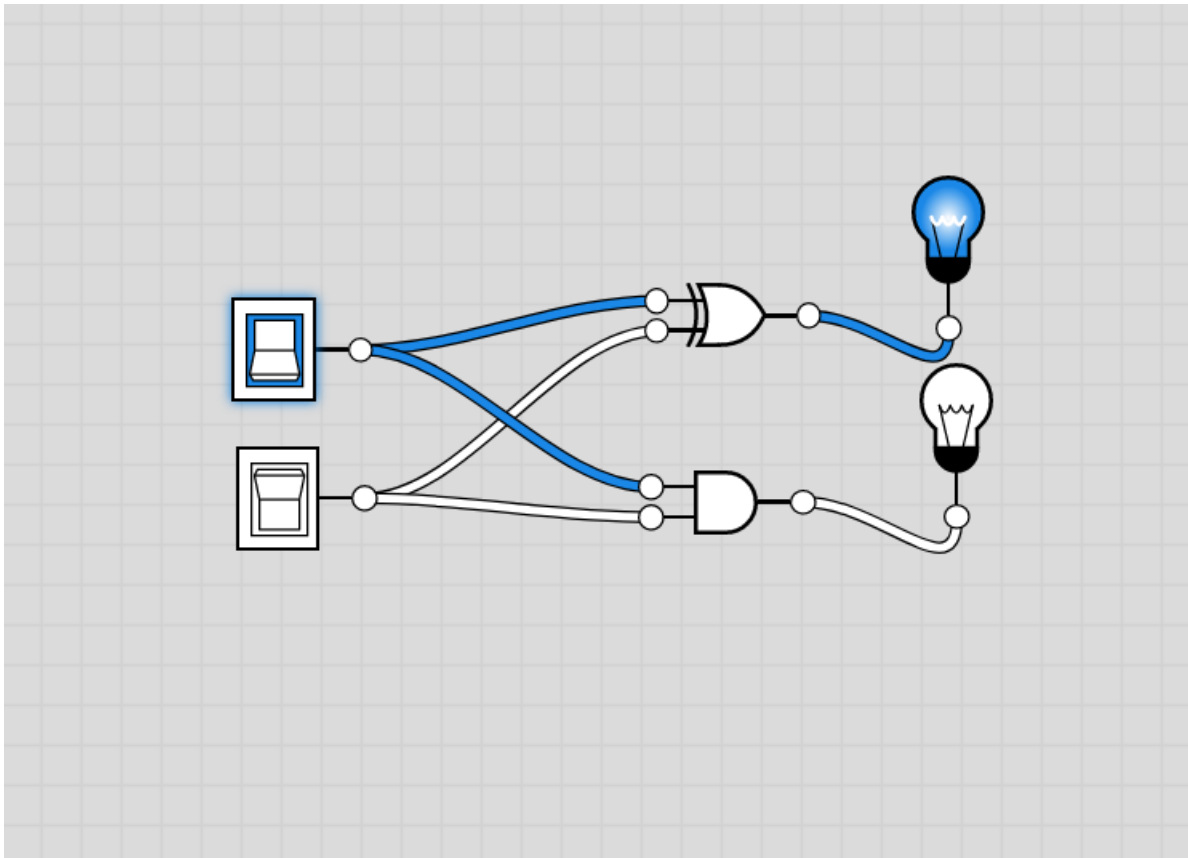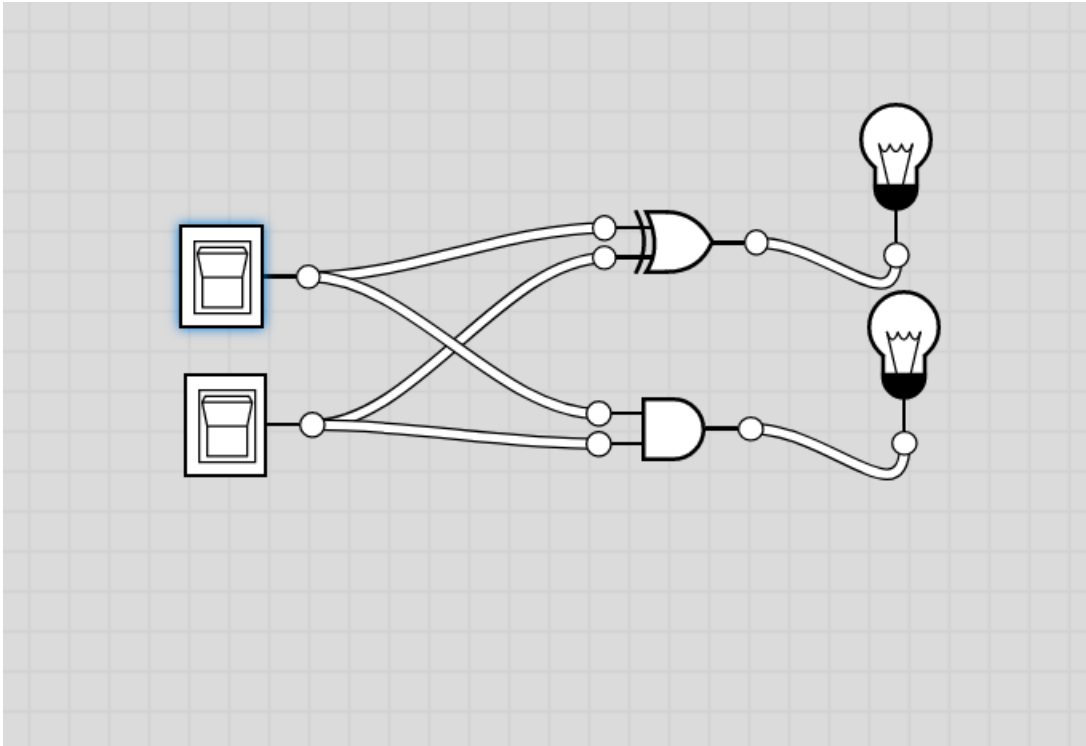d) Software Simulation (Show here your results for each combination that gives a high output)



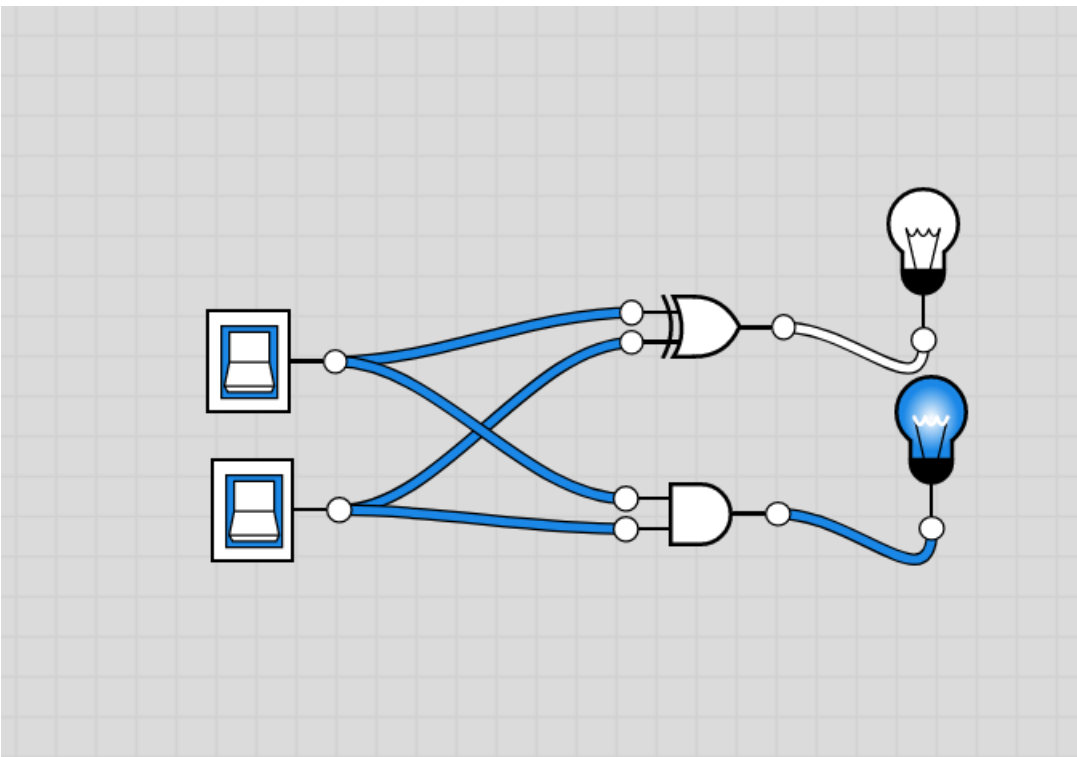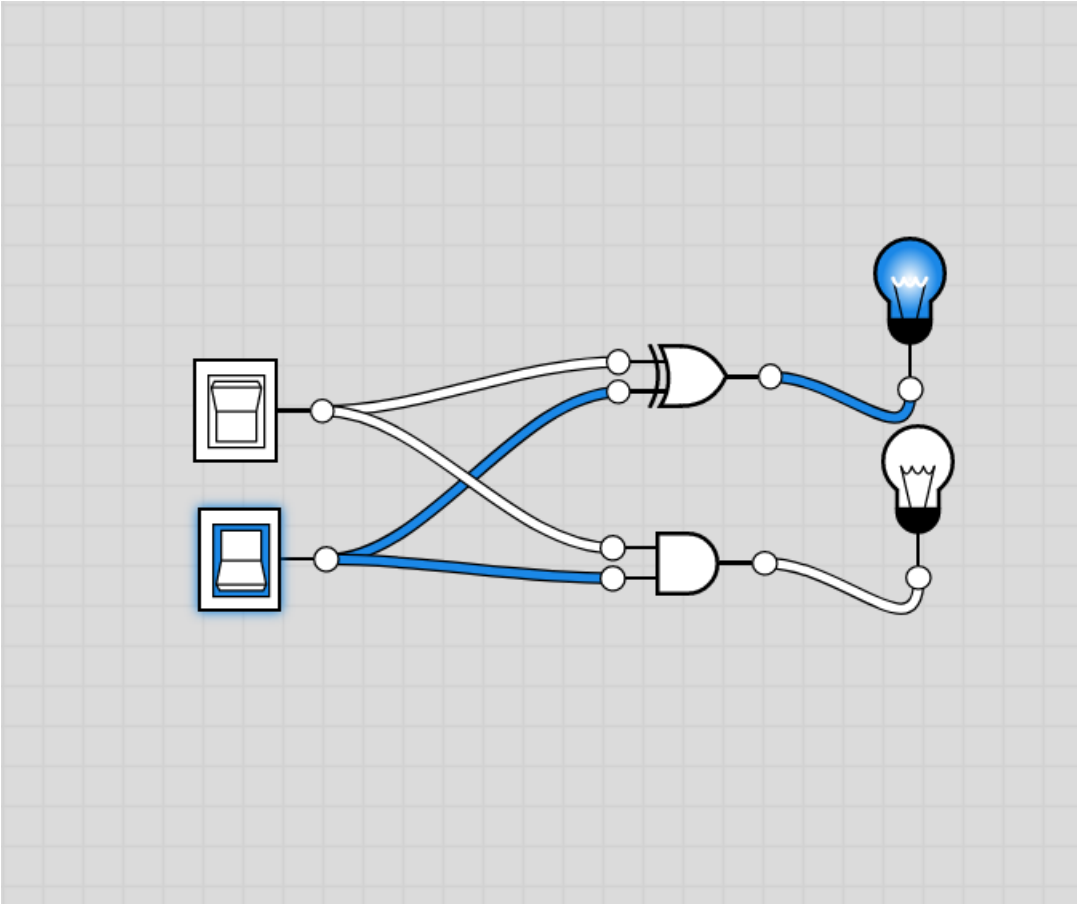

Full Adder


a) Truth Table

A	B	CIN	SUM	COUT
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


b) Boolean Expression (Simplified)



$$(A \text{ XOR } B) \text{ XOR } \text{CIN} = (A \oplus B) \oplus \text{CIN}$$




c) Logic Diagram

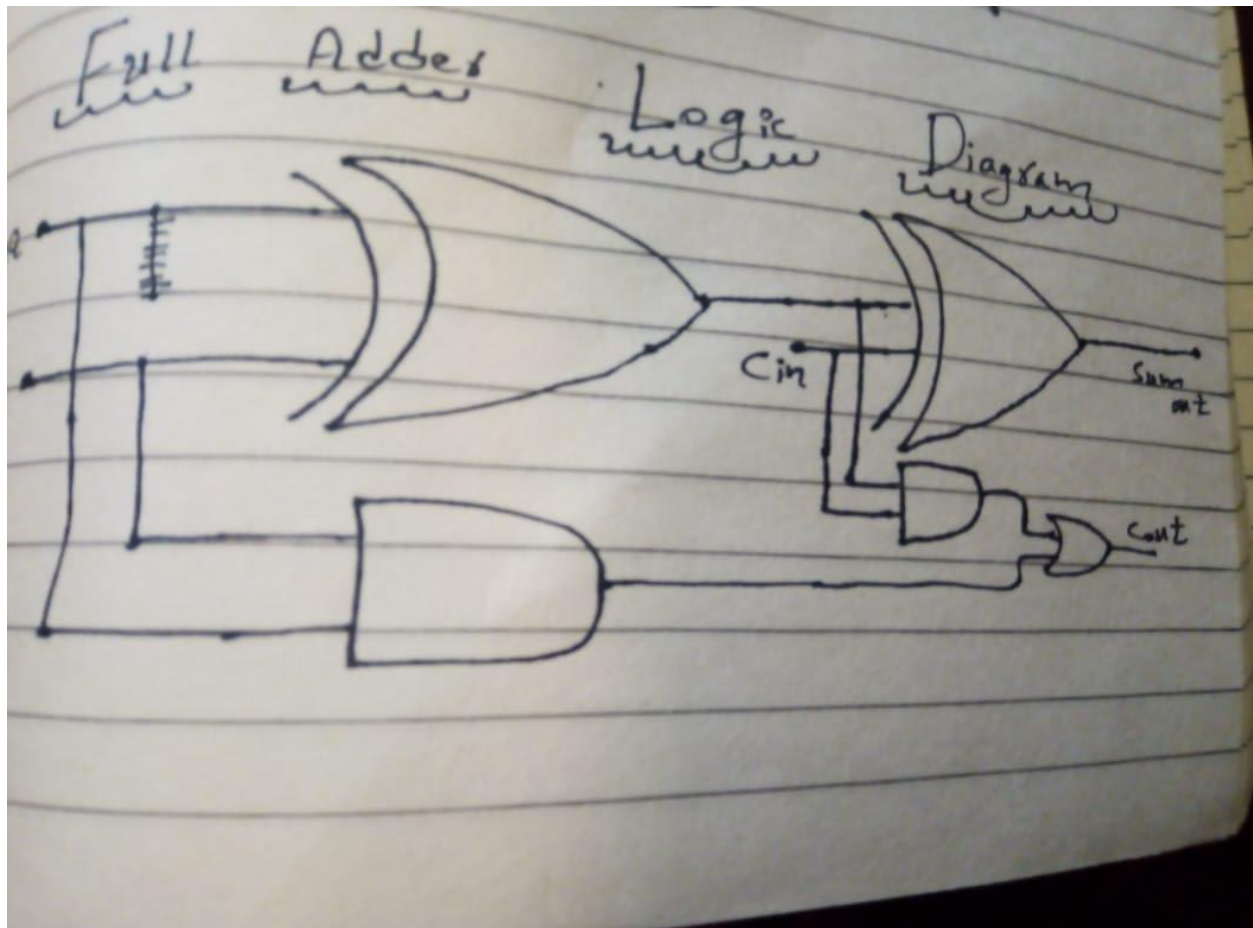


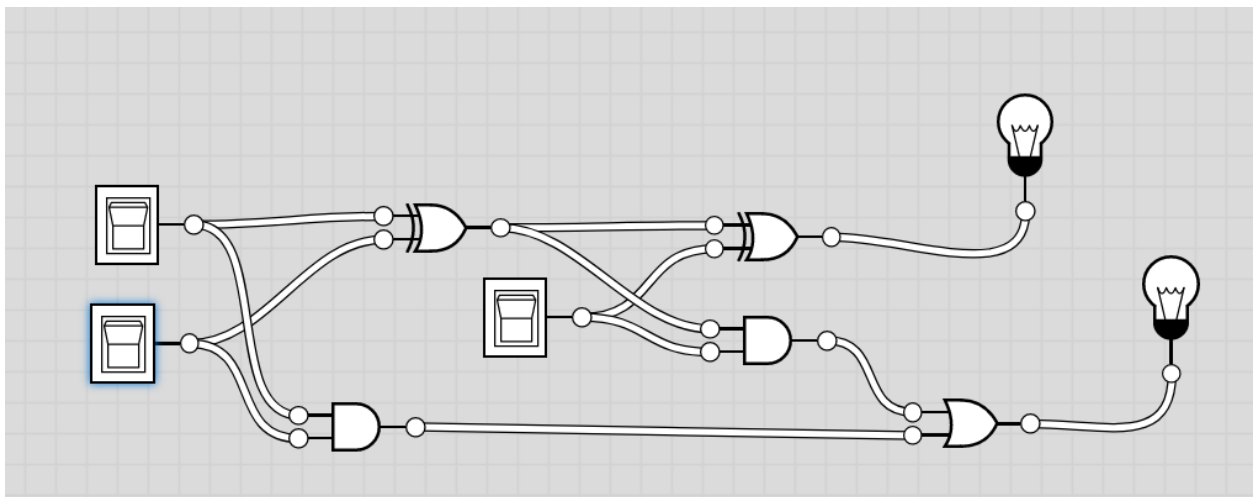- d) Software Simulation ([Show here your results for each combination that gives a high output](#))



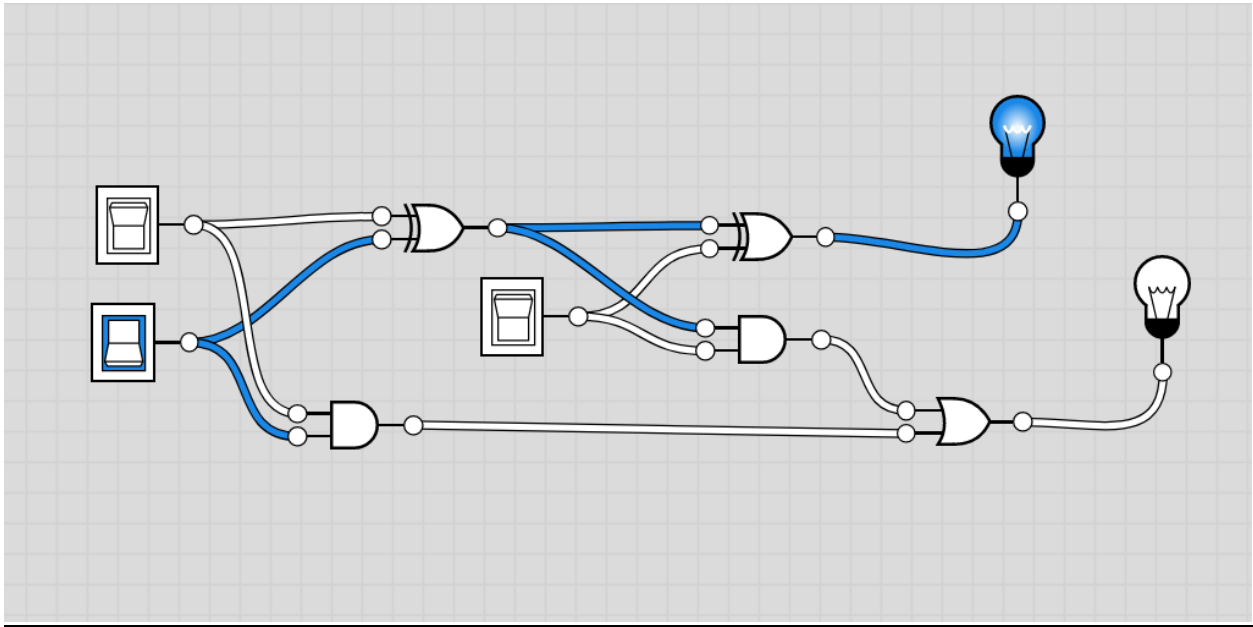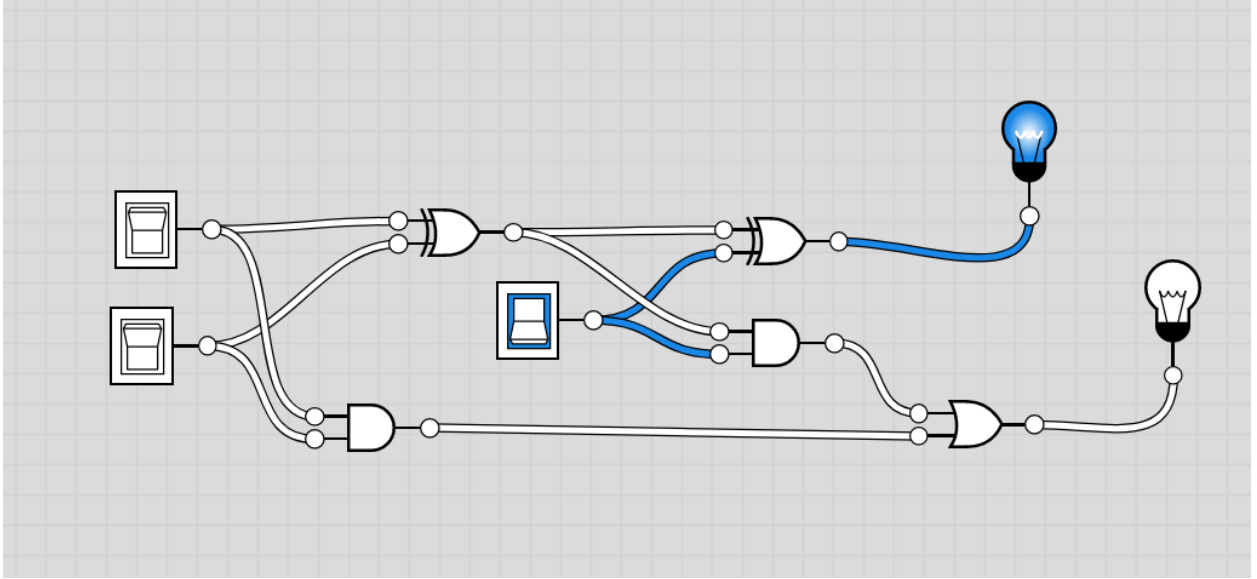

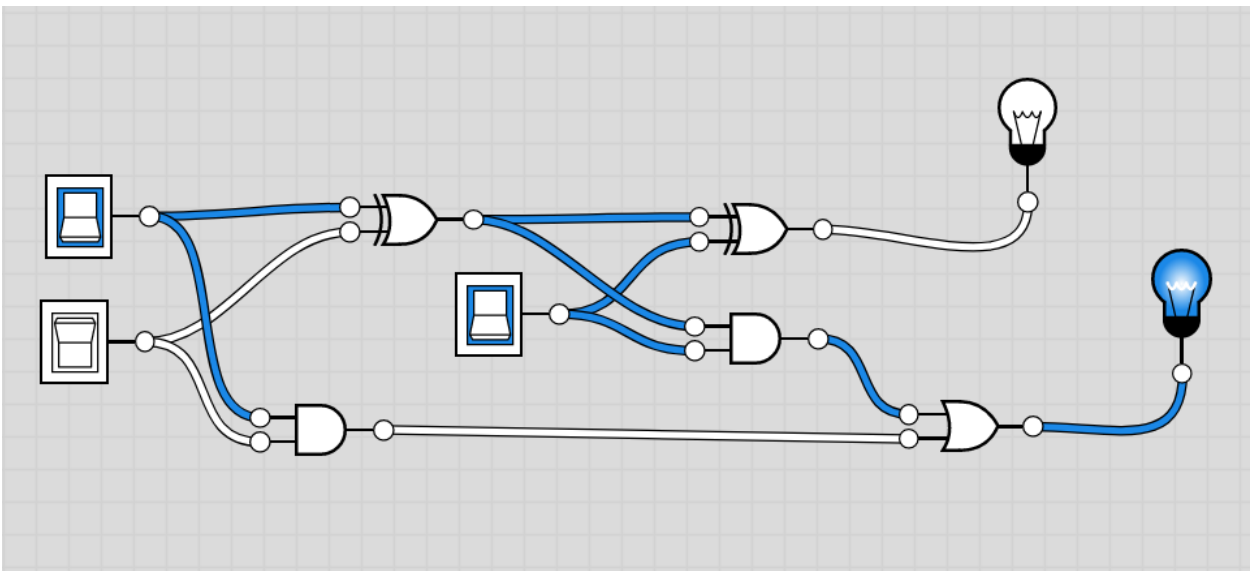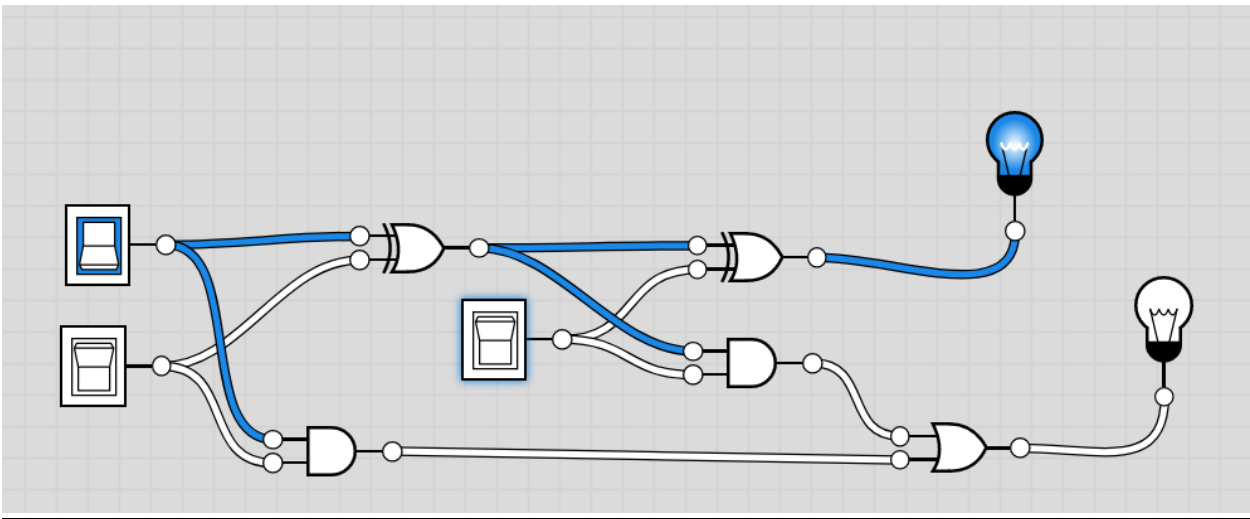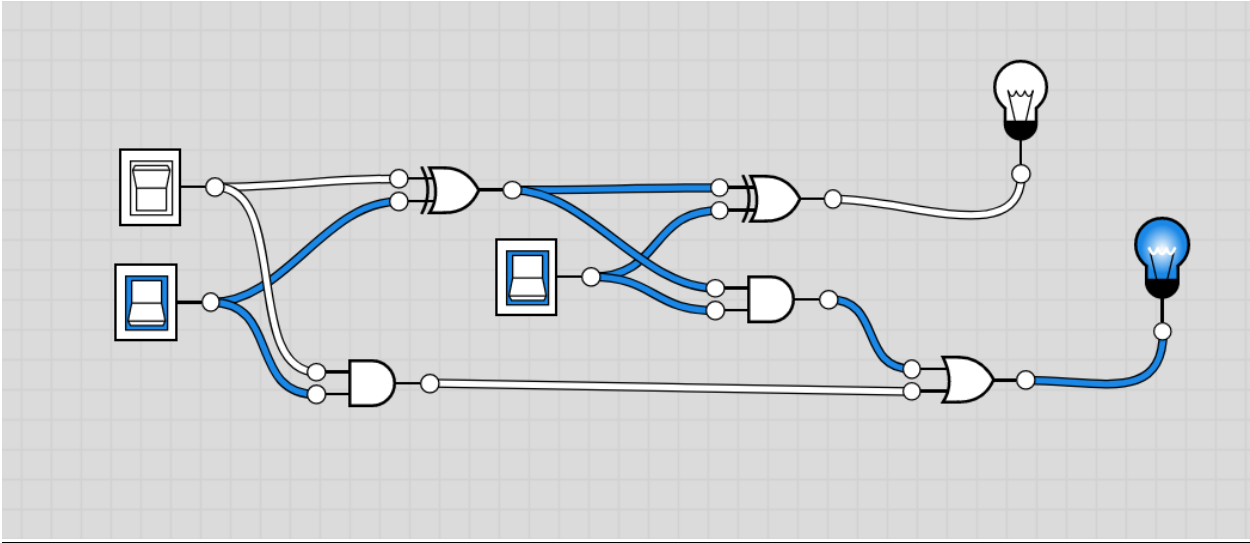


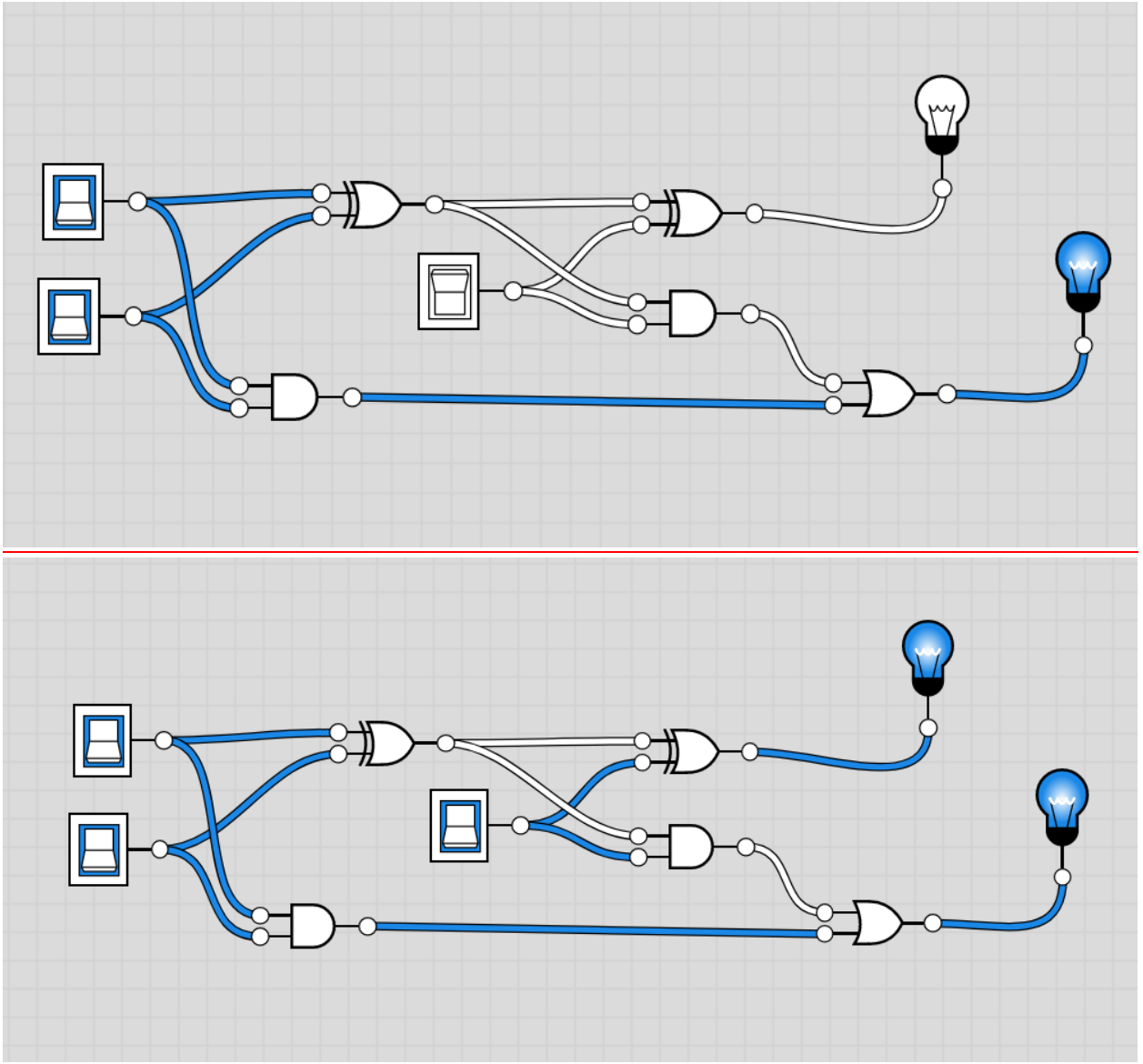


2. A full adder can be implemented using 2-half adders. Demonstrate the logic diagram for the said circuit. Simulate your circuit for the verification of results.

a) Logic Diagram of Full Adder using 2-Half Adders

Full Adder Using Half Adder

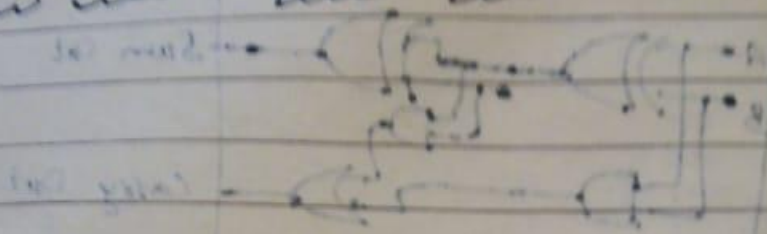

~~Full Adder~~

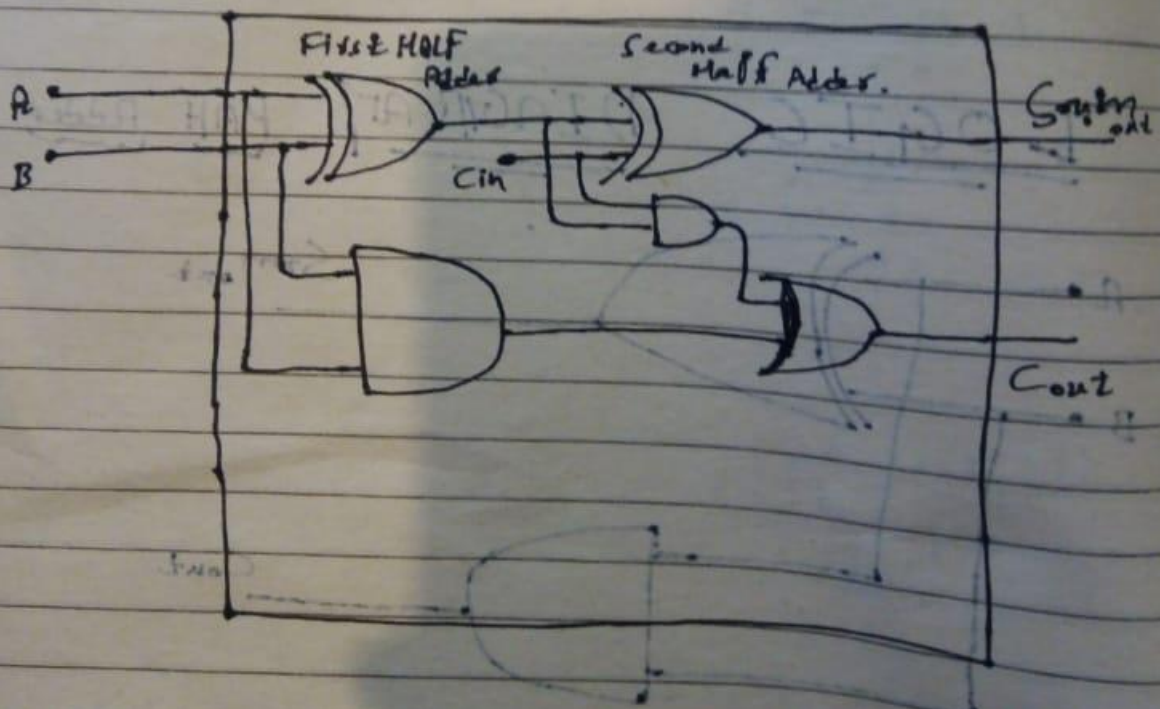

b) **Software Simulation** (Show here your results for each combination that gives a high output)

