

Lab 4

To Simplify Boolean Expressions and Implement Respective Digital Circuits Using Karnaugh Map


Note: For examples, refer to the following link: <https://www.geeksforgeeks.org/introduction-of-k-map-karnaugh-map>

Tasks

1. Construct K-Map for the function given below. Show the simplified output expression and verify the output with the help of software simulation.

$$Z = f(A, B) = \bar{A}\bar{B} + A\bar{B} + \bar{A}B$$

K-Map

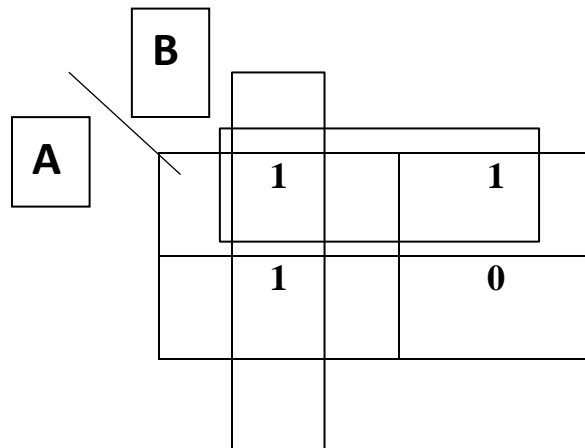



Simplified Output Function


$$F = A' + B'$$

Software Simulation of Logic Circuit From Simplified Function

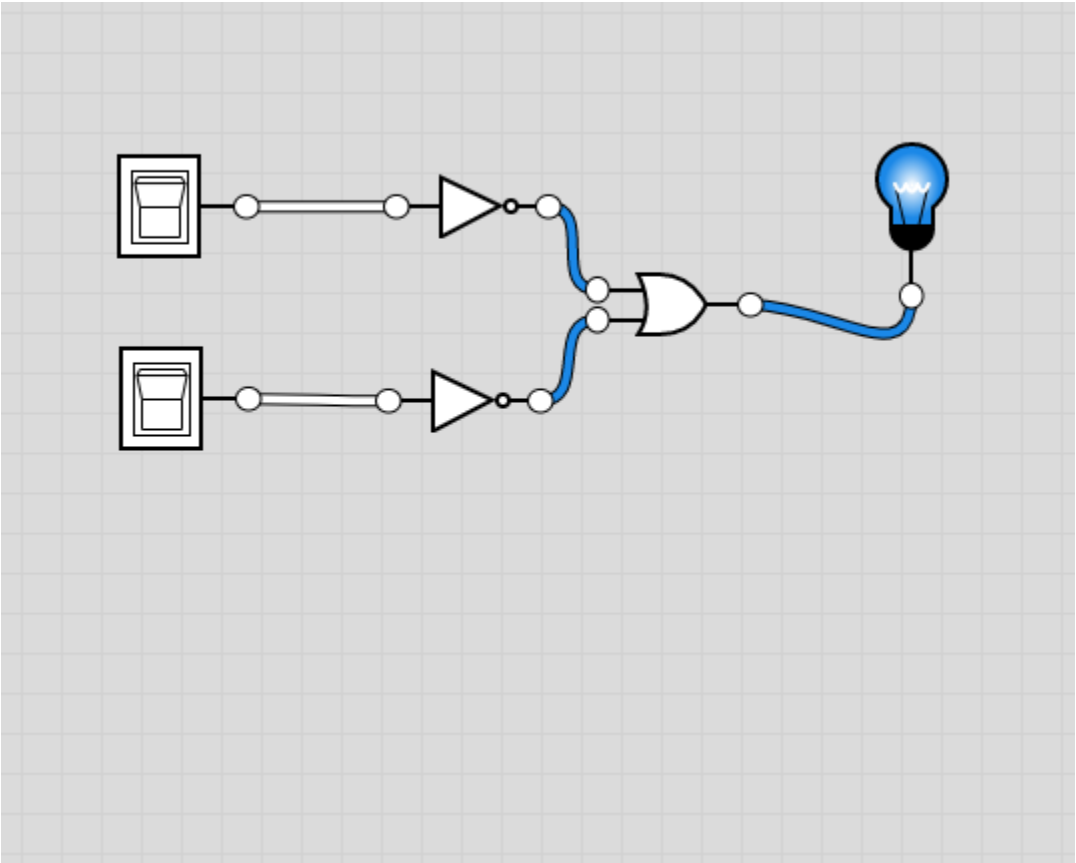(Show here your results for each combination that is present in the Boolean expression)



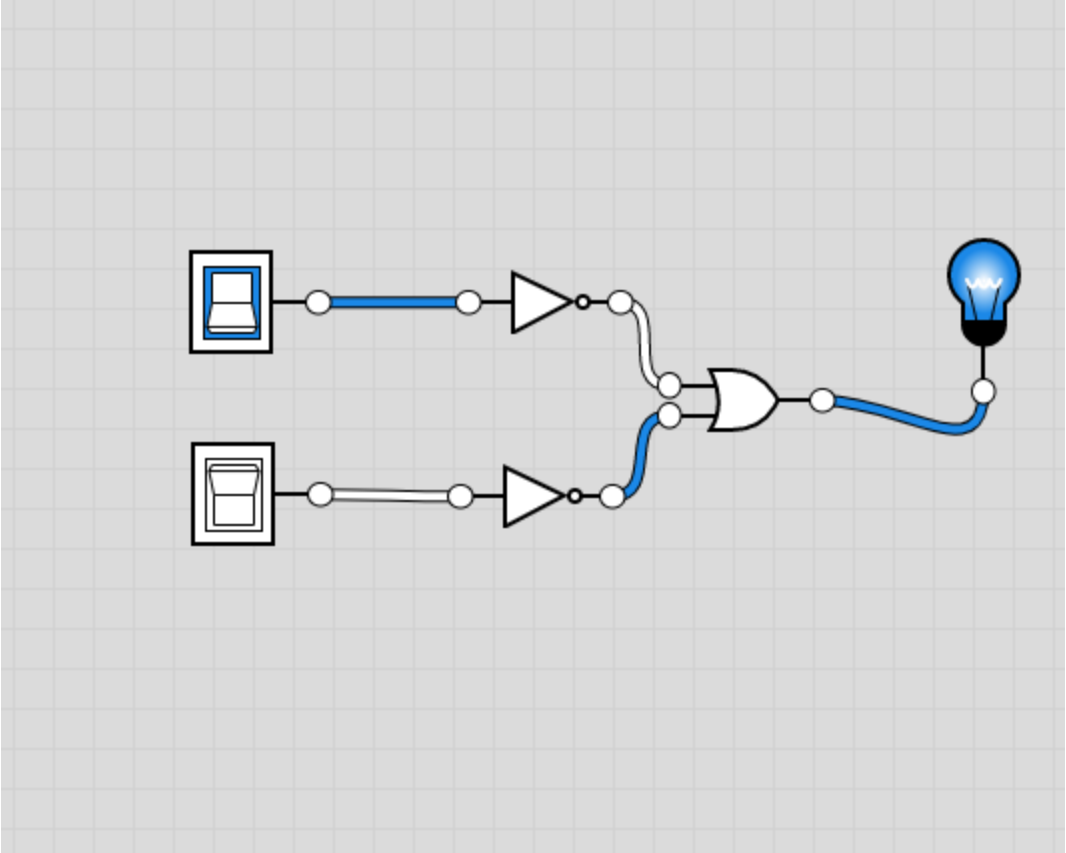

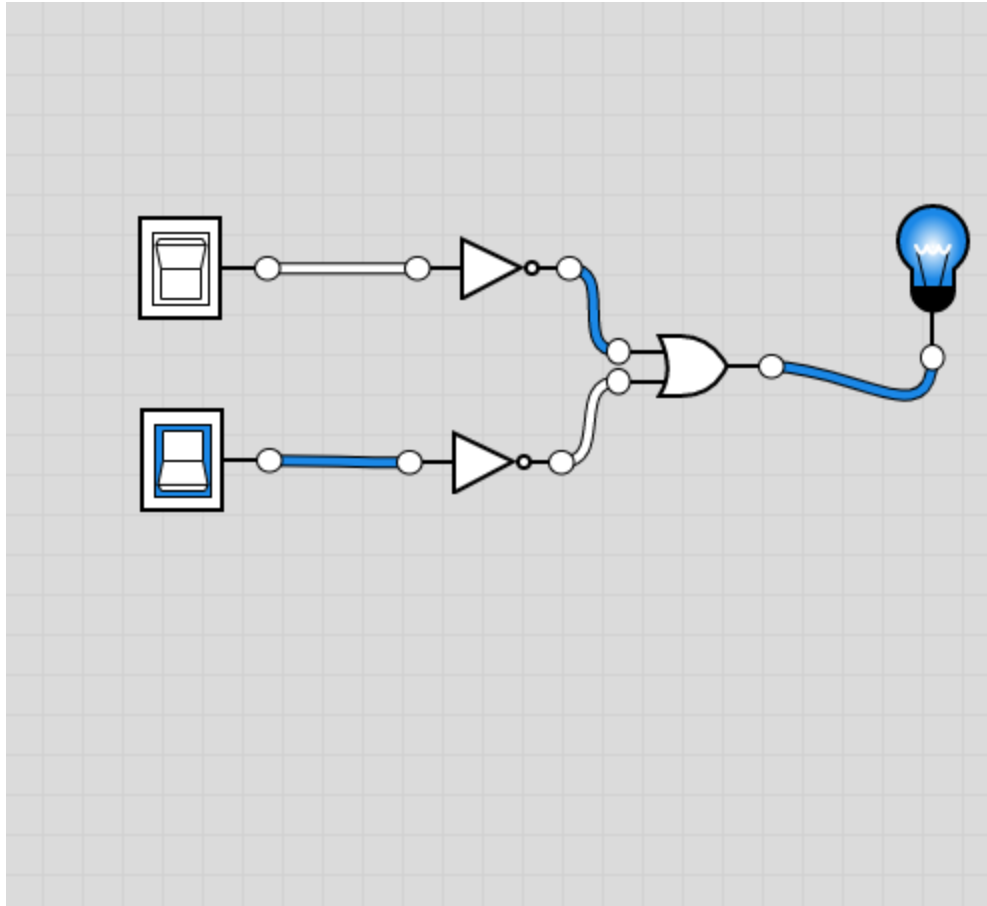

2. Minimize the following function using K-Map. Verify the output expression with the help of simulation.

$$f(a,b,c,d) = \sum m(3,7,11,12,13,14,15)$$

K-Map


<div>AB</div>	<div>CD</div>			<div>1</div>	
				<div>1</div>	
		<div>1</div>	<div>1</div>	<div>1</div>	<div>1</div>
				<div>1</div>	


Simplified Output Function

$$F = CD + AB$$

Software Simulation of Logic Circuit From Simplified Function

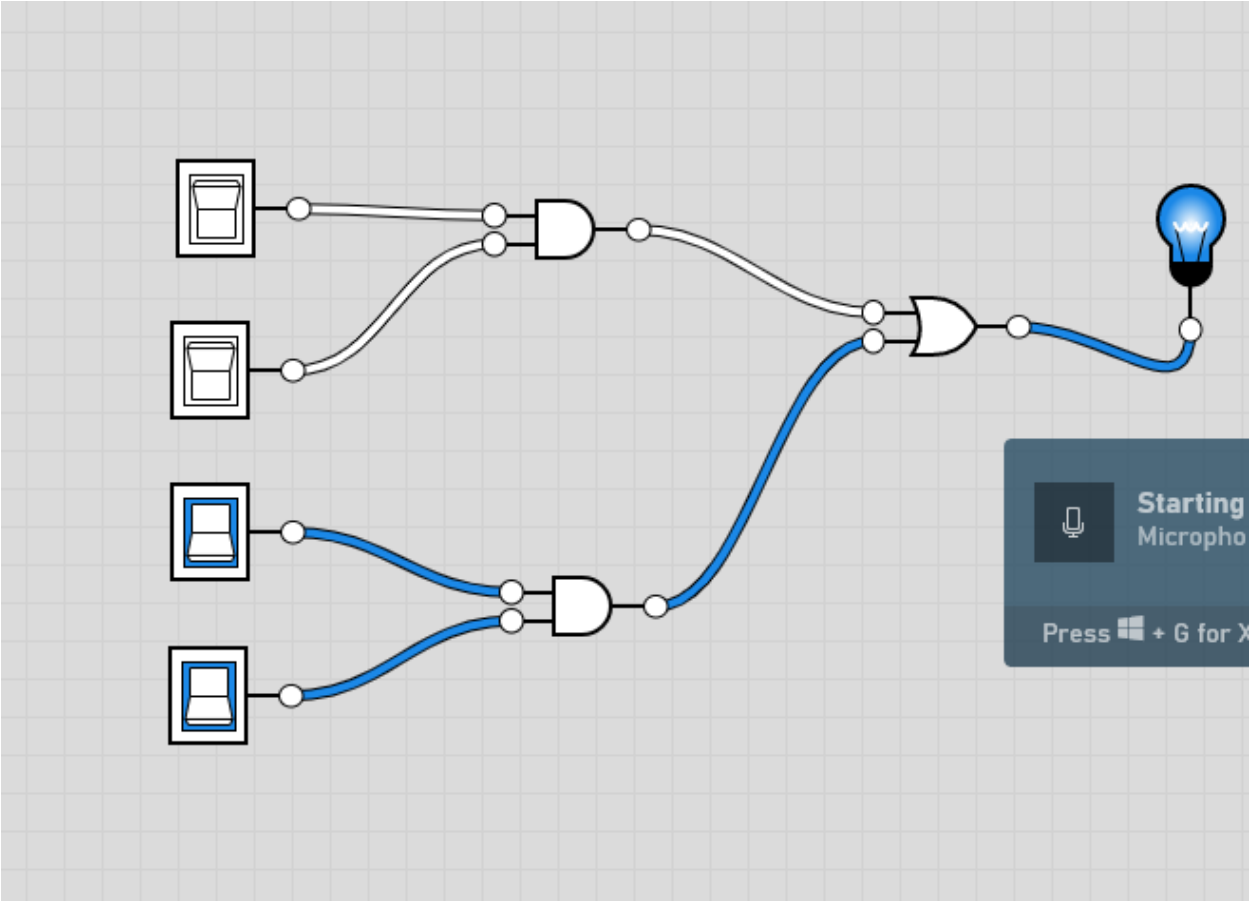(Show here your results for each combination that is present in the Boolean expression)



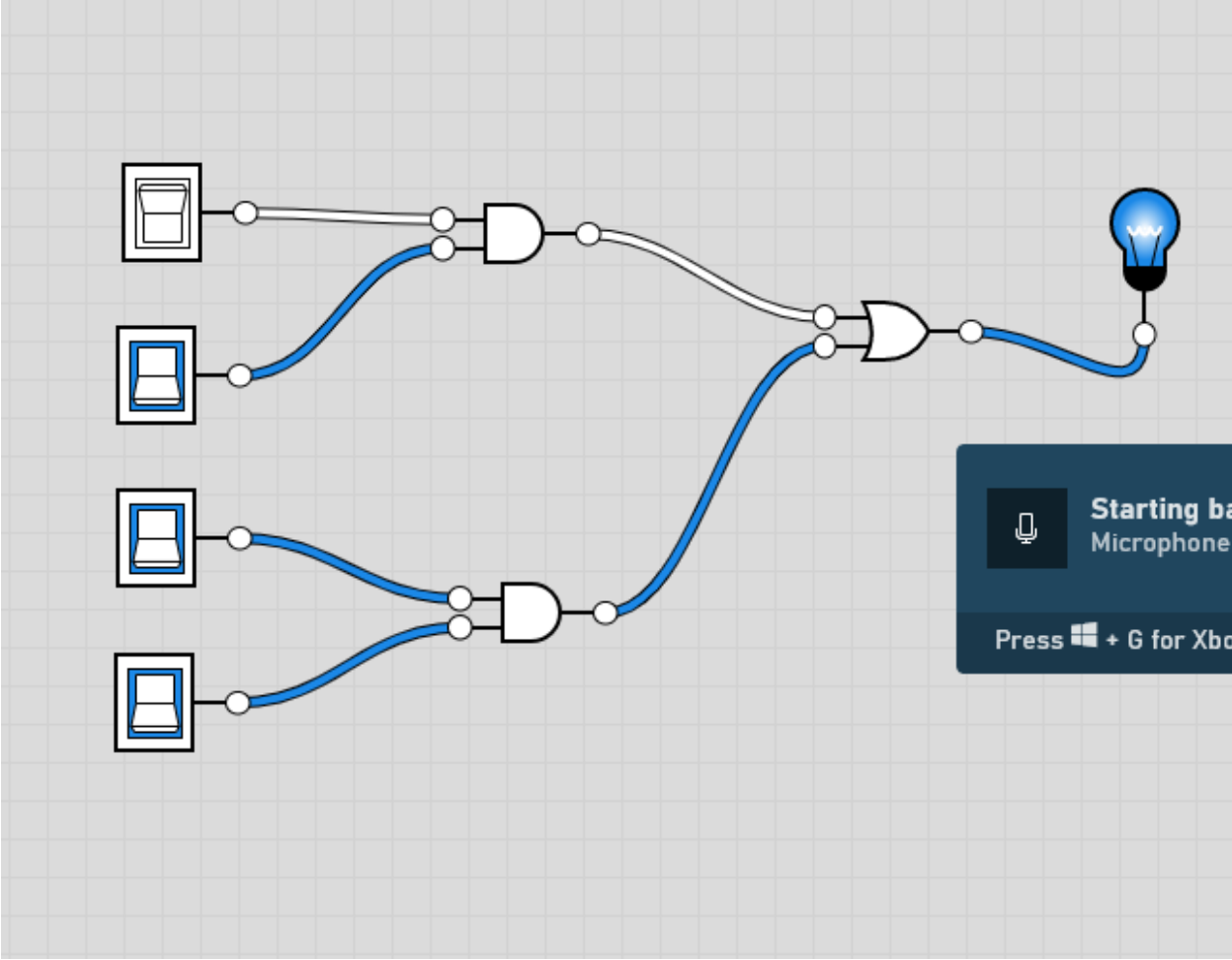

- 3. Construct K-Map for the given POS form given below. Simulate your final expression (reduced) and show the results.**

$$F(A,B,C,D)=\pi(3,5,7,8,10,11,12,13)$$

K-Map

The diagram shows a 4x4 grid with the following structure:

- AB**: A label in a box at the top left, with a diagonal line extending from its bottom-right corner towards the center of the grid.
- CD**: A label in a box at the top center.
- Grid Content**:


		0	
	0	0	
0	0		
0		0	0



Simplified Output Function


$$F = (C + D + A') \cdot (B' + C + D') \cdot (C' + D' + A) \cdot (A' + B + C')$$

Software Simulation of Logic Circuit From Simplified Function

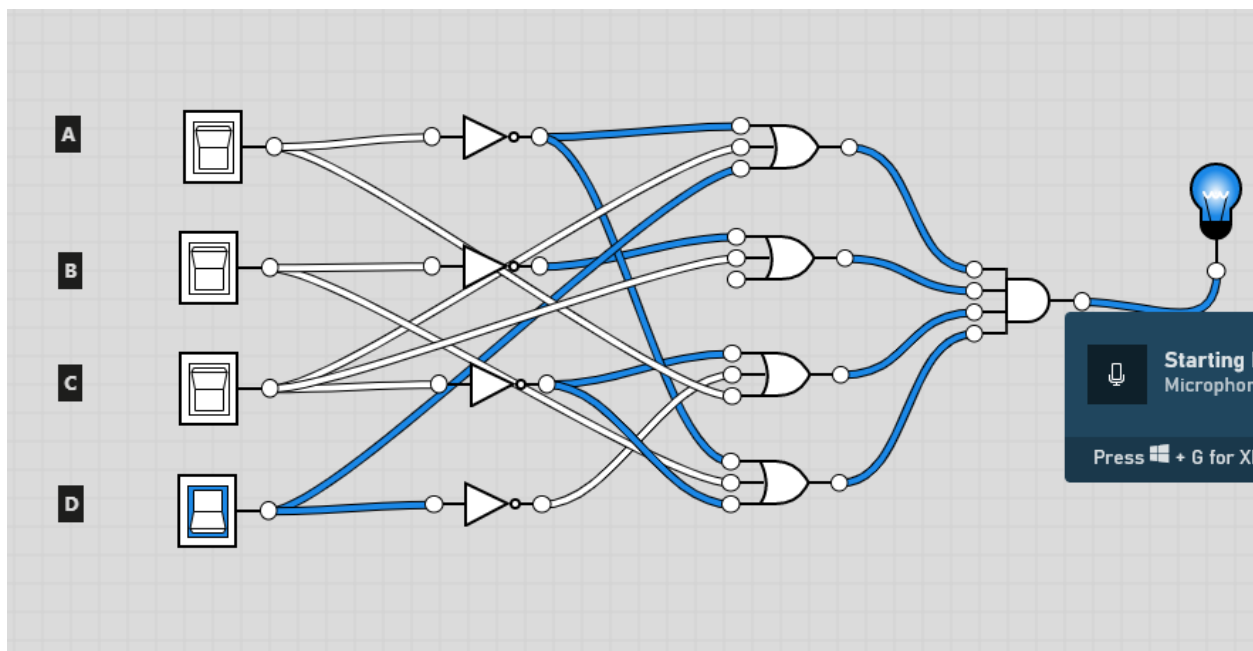(Show here your results for each combination that is present in the Boolean expression)



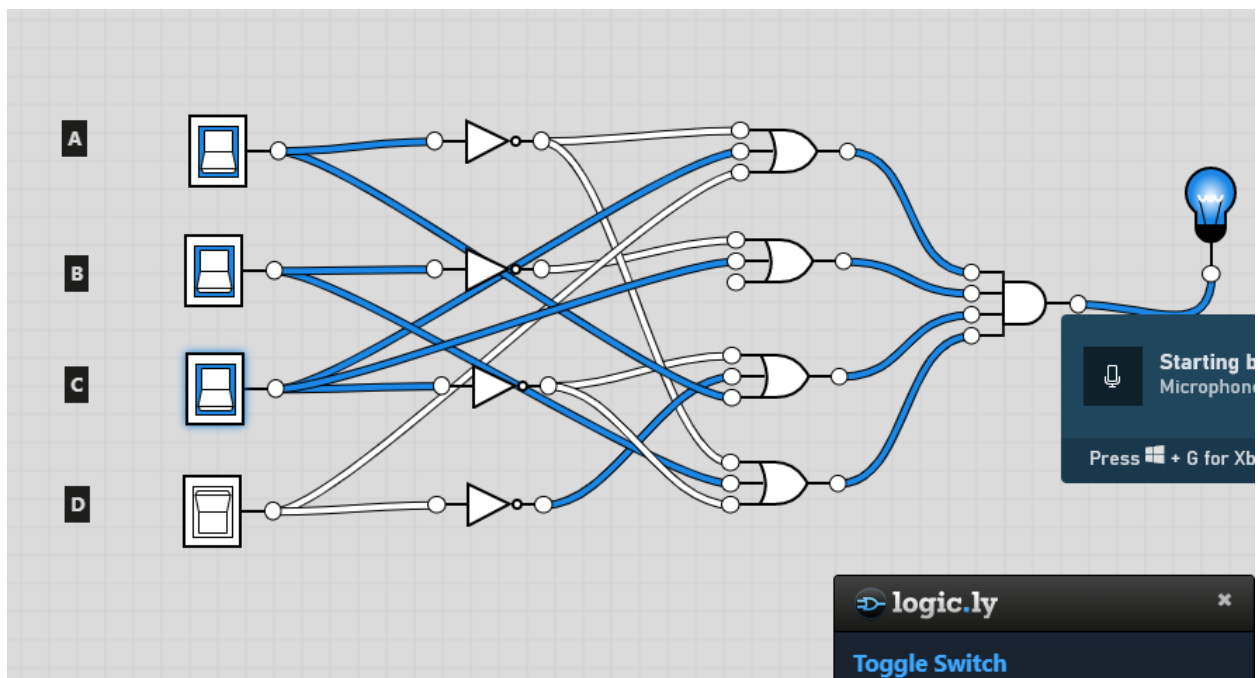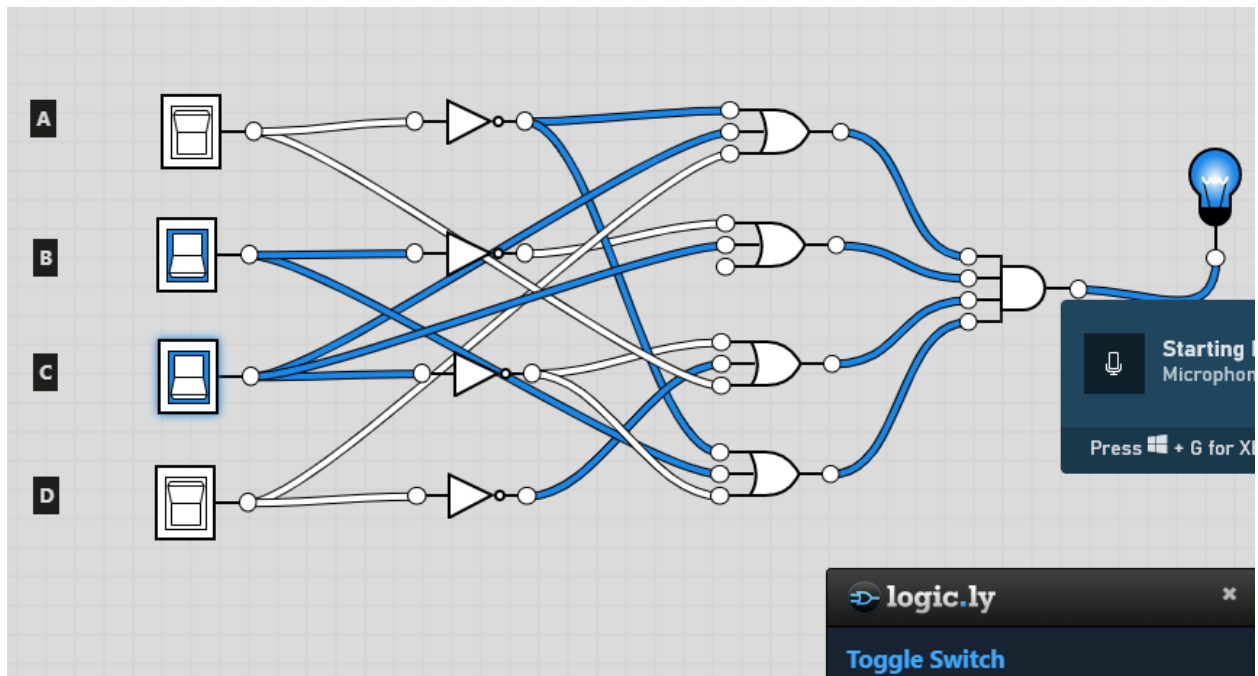


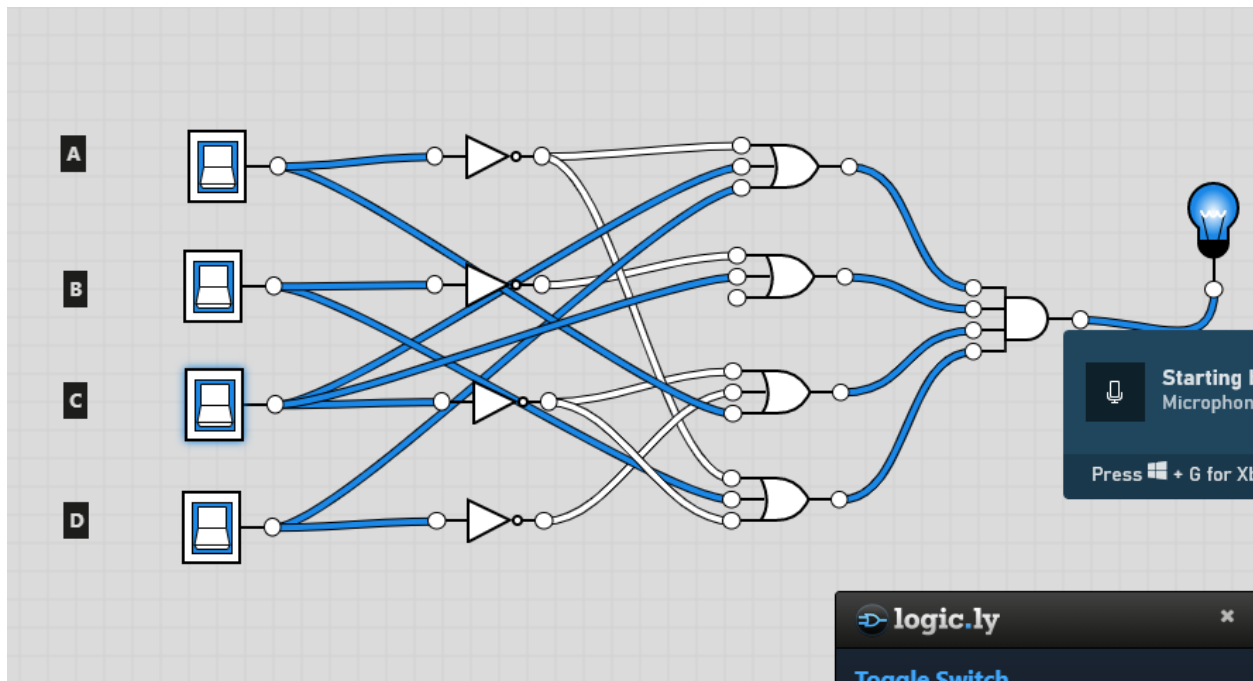

4. Devise a minimized expression for the given truth table using K-Map (SOP form).
- a)

A	B	C	Out
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

KMAP:

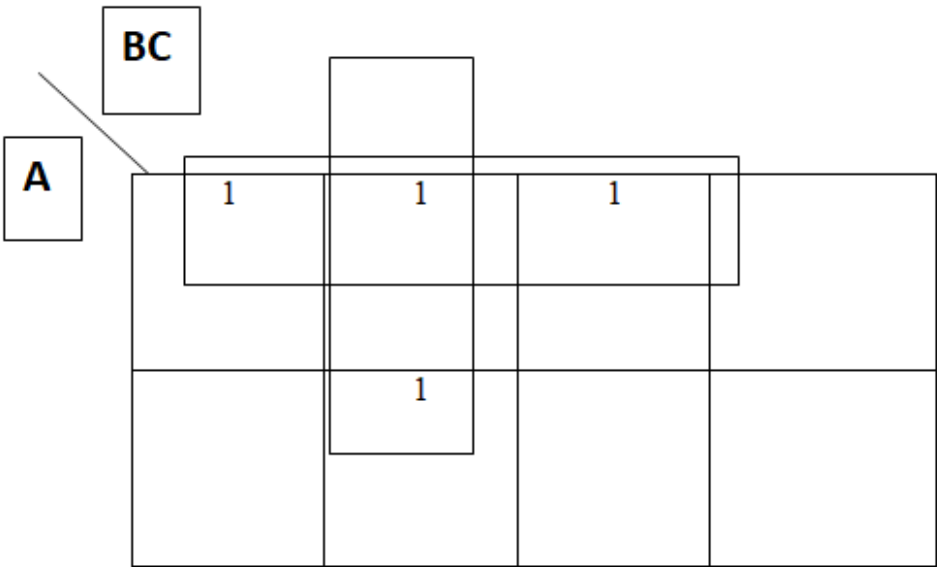


Expression

Out=

$$F = A' + B'C$$

b) For the above truth table, devise an expression in POS form using KMap.

K-Map

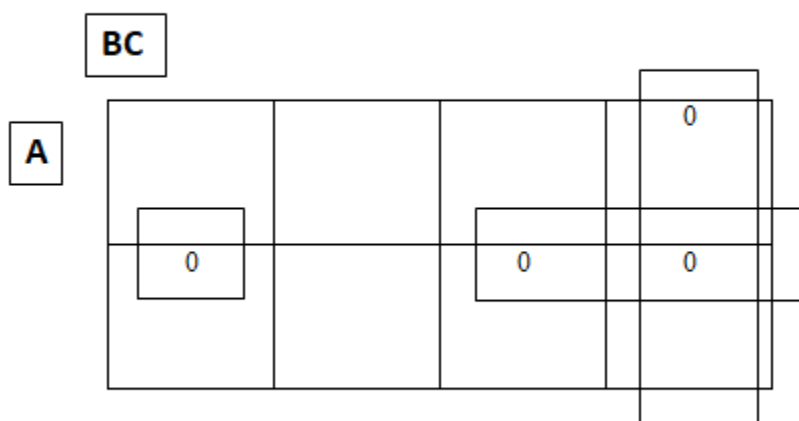

Expression

Out=

$$F = (A' + B + C) \cdot (A' + B') \cdot (B' + C)$$

c) Devise a truth table and Boolean expression for the given K-Map.

		CD			
		00	01	11	10
AB	00		1		
	01		1		
	11		1		
	10	1	1		1

Truth Table

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

Expression

$$F = (A'B'C'D) + (A'BC'D) + (AB'C'D') + (AB'C'D) + (AB'CD')$$

