

20P-0101

MUHAMMAD SHERJEEL

AKHTAR

DLD LAB

ASSIGNMENT

Submitted to MAAM ANAM

Lab 8

To Practice Binary to Gray Code & BCD to Excess-3 Conversion

Note: You may draw all the logic diagrams with hand and paste the pictures here. Also, the conversions in the tasks can be done by hand if doing it in soft seems difficult to you.

*Use Logicly software with your name, roll number & section mentioned in your workspace. Make sure that all of your connections are clearly visible and distinguishable. In logicly, use **“text”** label to point out/show all your inputs & outputs.*

Task 1

- a) Convert the given binary codes into respective gray codes. Mention each step while converting the codes.


1111, 1101, 1001, 010, 011, 110

(X) DLD-Lab


Q. Binary codes to gray code:

① $(1111)_2$


MSB

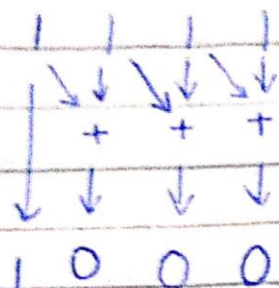


② $(1101)_2$

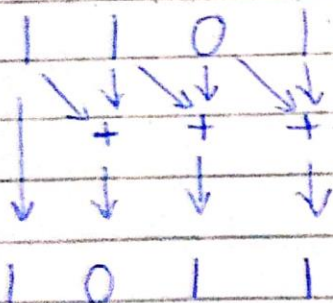


② $(1001)_2$

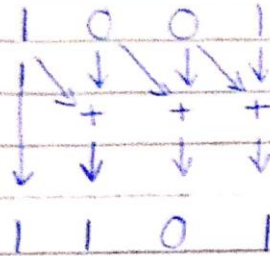


④ $(010)_2$

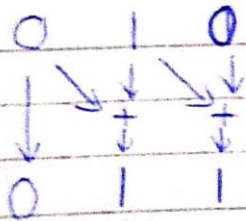

⑤ $(011)_2$

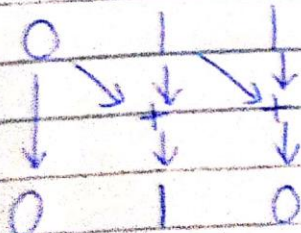

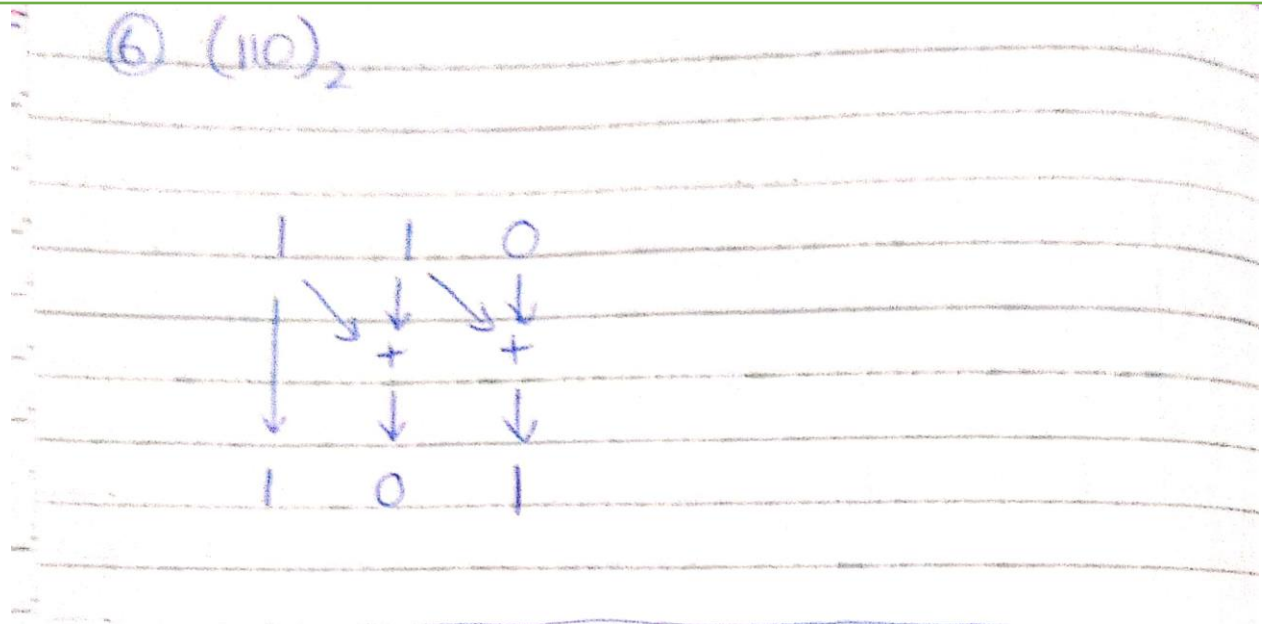


b) Convert the given gray codes into respective binary codes. Mention each step while converting the codes.


1011, 0101, 1100, 0100

Q2, Gray codes to binary codes:


① $(1011)_G$

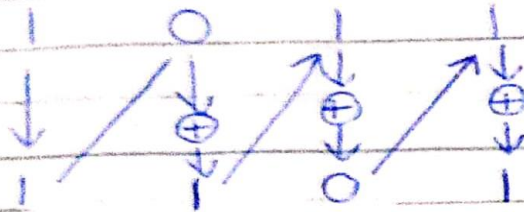


② $(0101)_G$

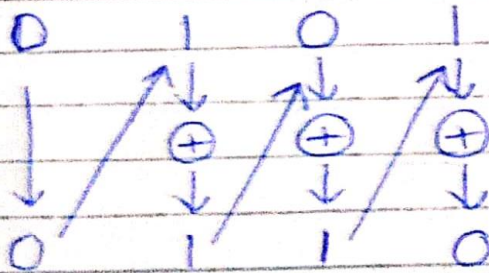

③ $(1100)_4$

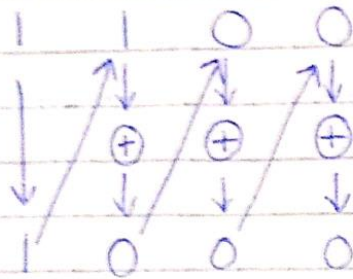

④ $(0100)_4$

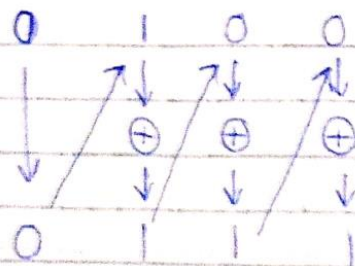

Task 2

Devise a truth table for 3-bit Binary to Gray code converter. Write simplified logical expressions and simulate the logic diagram in Logicy software to verify your results. Show KMap simplification as well.

a) Truth Table

A	B	C	G2	G1	G0
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	1
0	1	1	0	1	0
1	0	0	1	1	0
1	0	1	1	1	1
1	1	0	1	0	1
1	1	1	1	0	0

b) Boolean Expression (Simplified using KMap)

KMap for G2


A	BC			
	1	1	1	1

$$G2 = A$$

KMap for G1

A	BC			
		1		1
		1		1

$$G1 = AB' + A'B$$

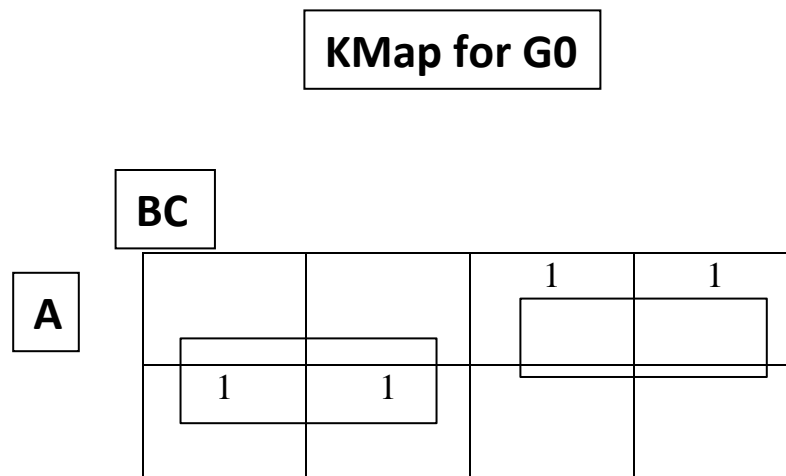

$$G0 = B'C + BC'$$

Simplified expression for G2, G1 and G0 is:


$$G2 = A$$

$$G1 = AB' + A'B$$

$$G0 = B'C + BC'$$


c) Logic Diagram



20P-0101, Muhammad Sherjeel Akhtar


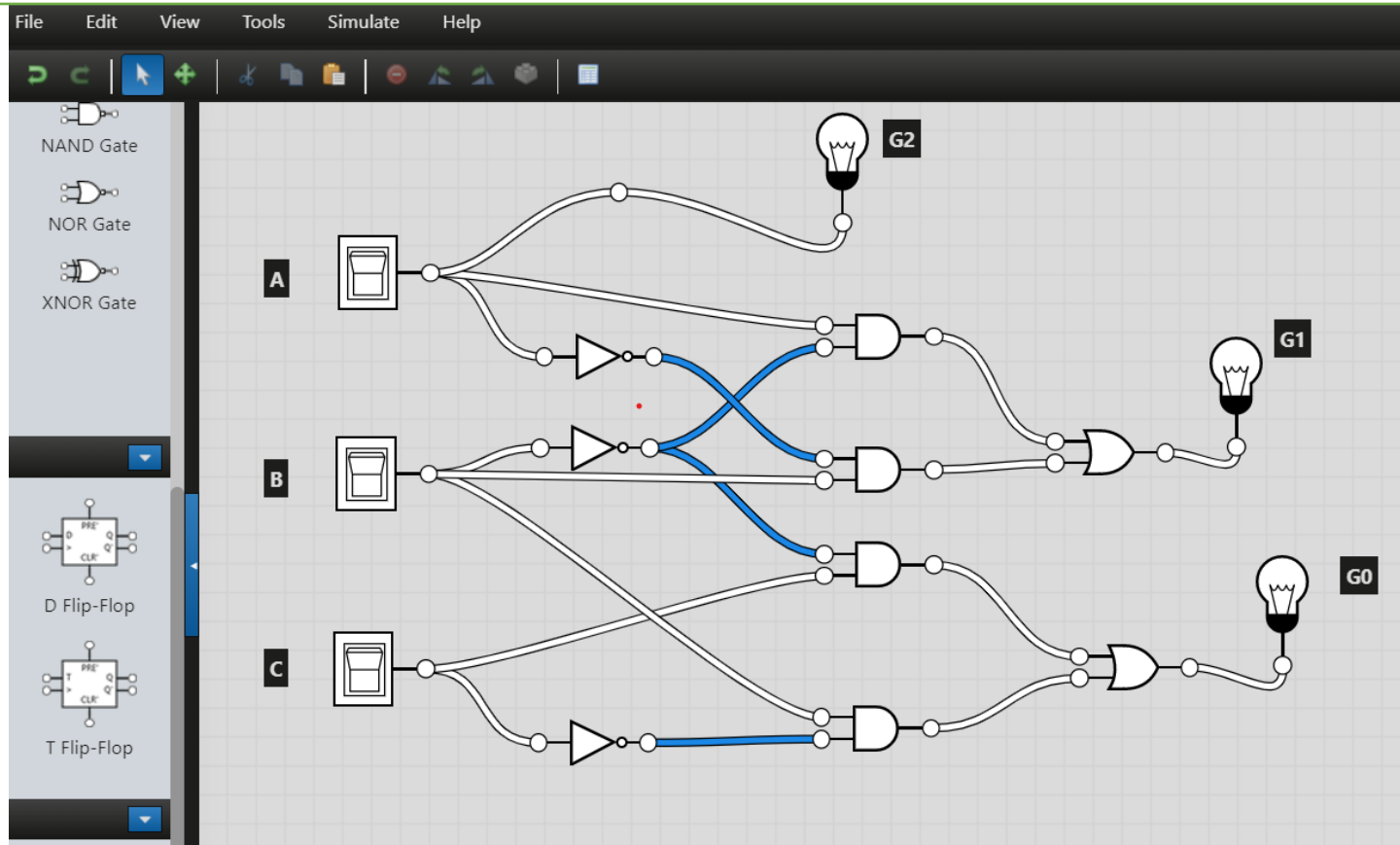


d) Software Simulation ([Show here your results for a few combinations to verify the circuit](#))

20P-0101, Muhammad Sherjeel Akhtar

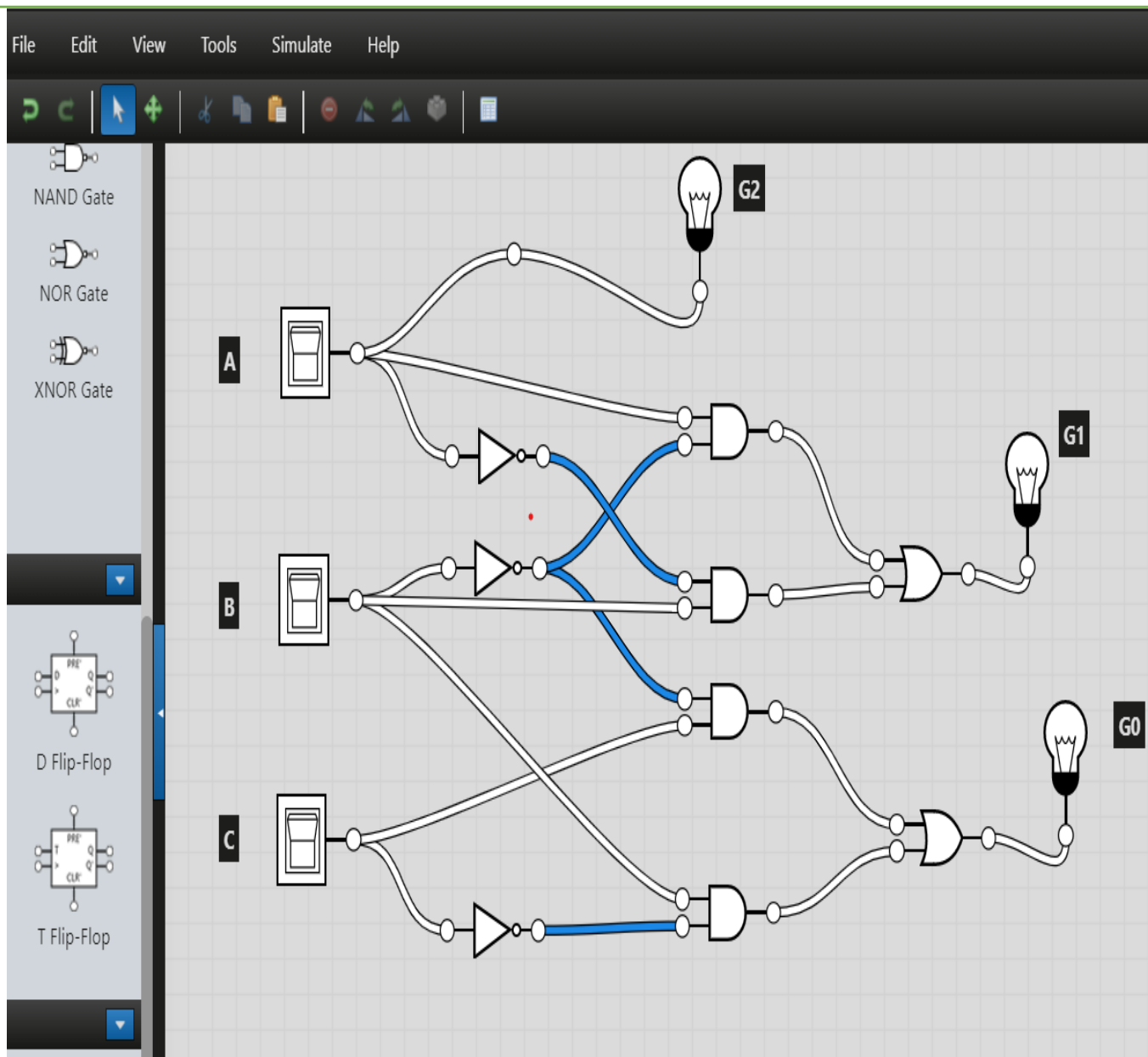

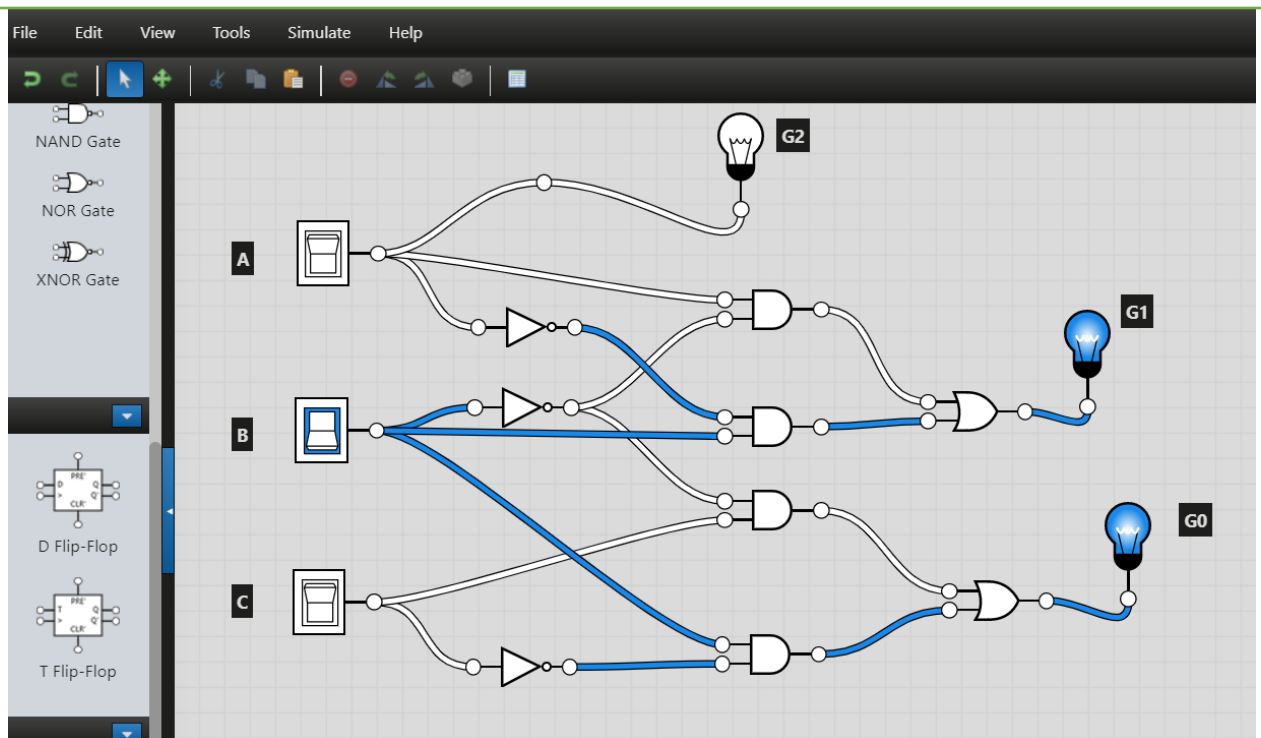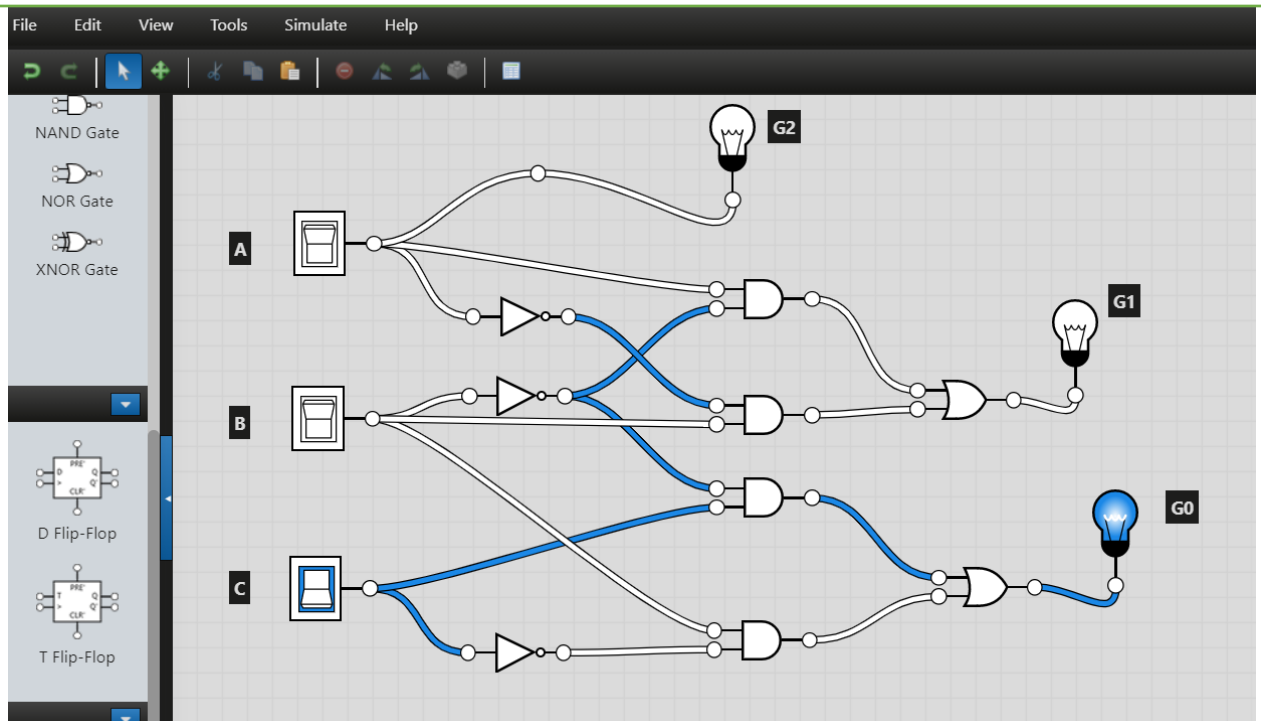

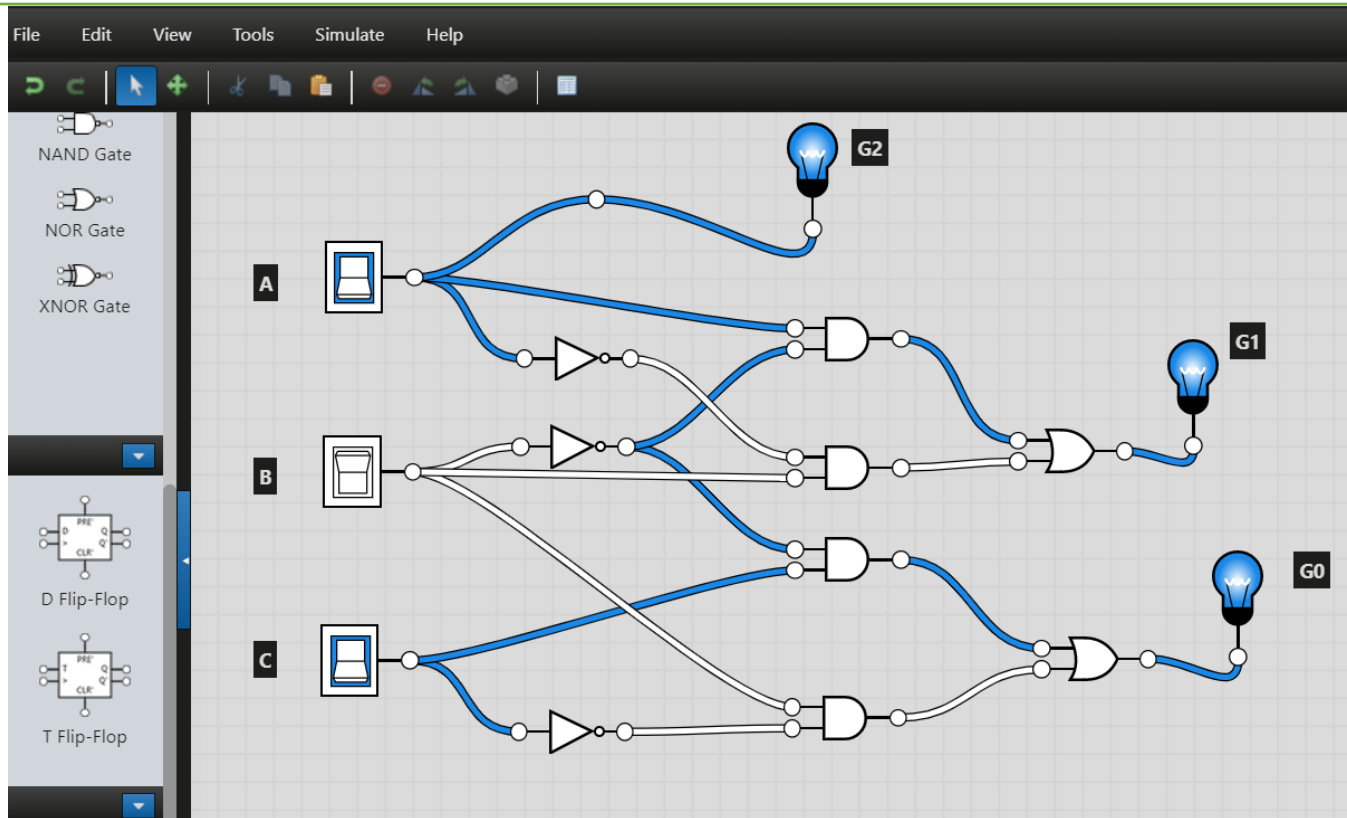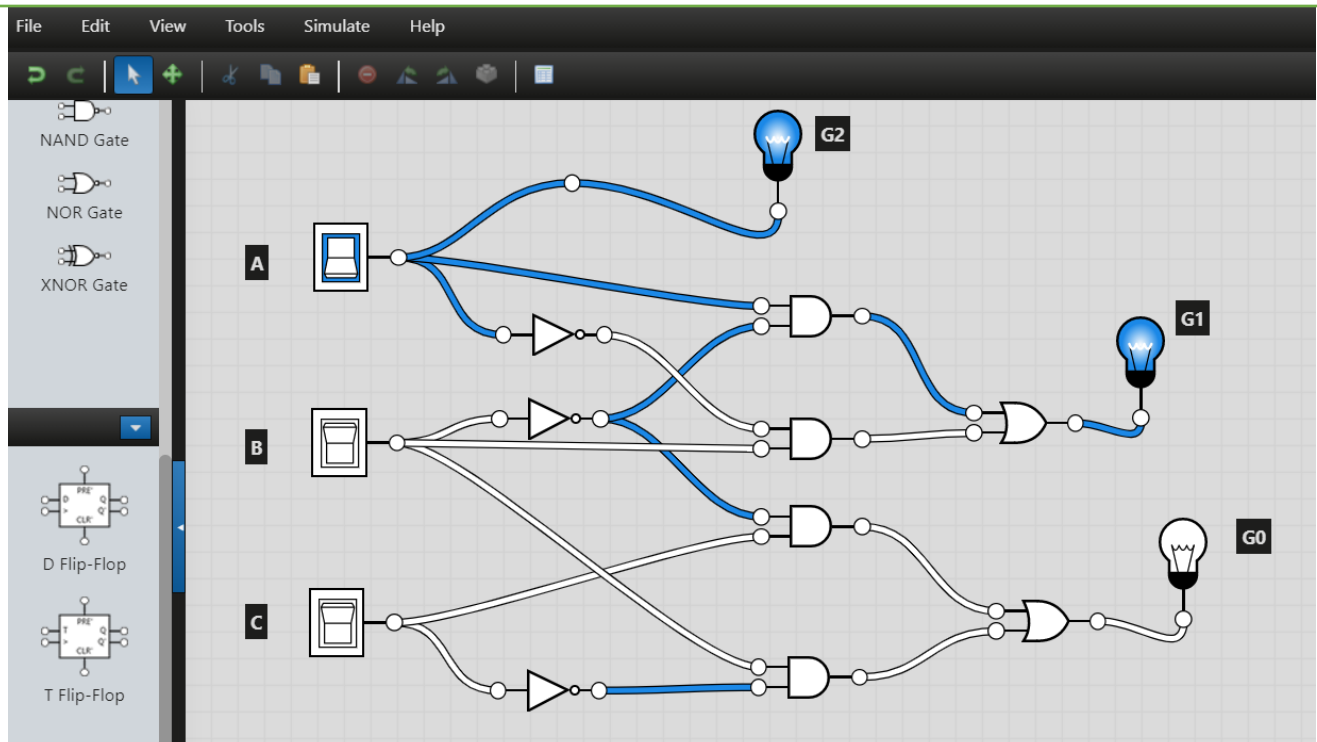

Task 3

- a) For the given numbers, find excess-3 codes. Mention all the steps of conversion.

4, 9, 25, 50, 250, 405.

Q3, a) Excess-3 code:

① 4:

$$4 = (0100)_{BCD}$$

$$\begin{array}{r} 0100 \\ 0011 \\ \hline 0111 \end{array}$$

$$4 = (0111)_{E-3}$$

② 9:

$$9 = (1001)_{BCD}$$

$$\begin{array}{r} 1001 \\ 0011 \\ \hline 1100 \end{array}$$

$$9 = (1100)_{E-3}$$

③ 25:

$$25 = (0010 \ 0101)_{BCD}$$

$$\begin{array}{r} 0010 \quad 0101 \\ 0011 \quad 0011 \\ \hline 0101 \quad 1000 \end{array}$$

$$25 = (0101 \ 1000)_{E-3}$$

④ 50:

$$50 = (0101 \ 0000)_{BCD}$$

$$\begin{array}{r} \textcircled{0}\textcircled{0}\textcircled{0} \\ 0101 \ 0000 \\ \underline{0011 \ 0011} \\ 1000 \ 0011 \end{array}$$

$$50 = (1000 \ 0011)_{E-3.}$$

⑤ 250:

$$250 = (0010 \ 0101 \ 0000)_{BCD}$$

$$\begin{array}{r} \textcircled{0} \quad \textcircled{0}\textcircled{0}\textcircled{0} \\ 0010 \ 0101 \ 0000 \\ \underline{0011 \ 0011 \ 0011} \\ 0101 \ 1000 \ 0011 \end{array}$$

$$(250) = (0101 \ 1000 \ 0011)_{E-3}$$

④ 405:

$$405 = (0100 \quad 0000 \quad 0101)_{\text{BCD}}$$

$$\begin{array}{r}
 0100 \quad 0000 \quad \overset{\overset{000}{}}{0101} \\
 0011 \quad 0011 \quad 0011 \\
 \hline
 0111 \quad 0011 \quad 1000
 \end{array}$$

$$405 = (0111 \quad 0011 \quad 1000)_{\text{E-3}}$$


- b) Devise a truth table for BCD to Excess-3 conversion (as discussed in the lecture). Write simplified expressions and simulate the logic circuit in Logically software to verify your truth table. You may paste screenshots of a few combinations from the truth table to check your circuit. Show your KMap simplification as well.

BCD to Excess-3 Converter

a) Truth Table


BCD (8421)				Excess- 3			
A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

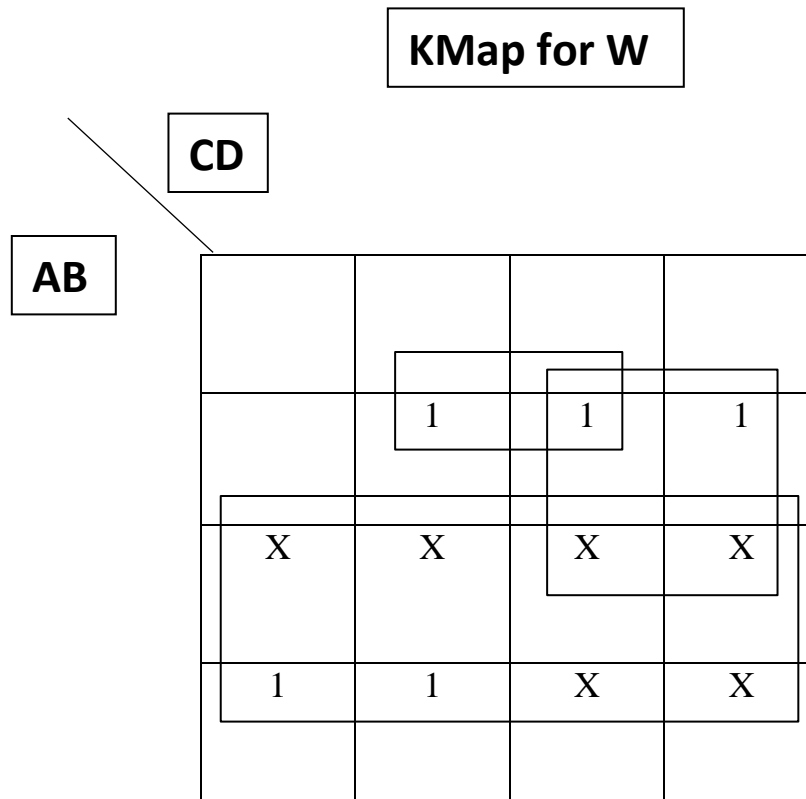b) Boolean Expression (Simplified Using KMap)




$$W = A + BC + BD$$

KMap for X

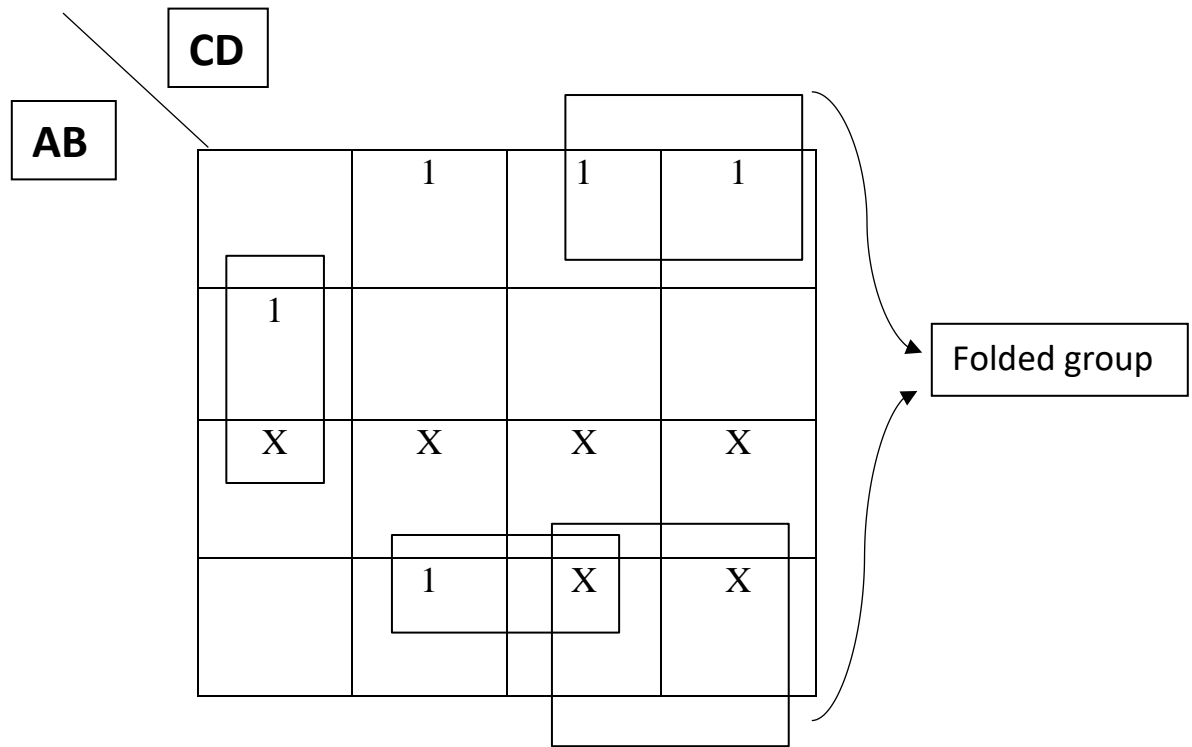

$$X = B'C + B'D + BC'D'$$


KMap for Y

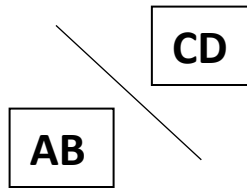

1		1	
1		1	
X	X	X	X
1		X	X

$$Y = CD + C'D'$$


KMap for Z

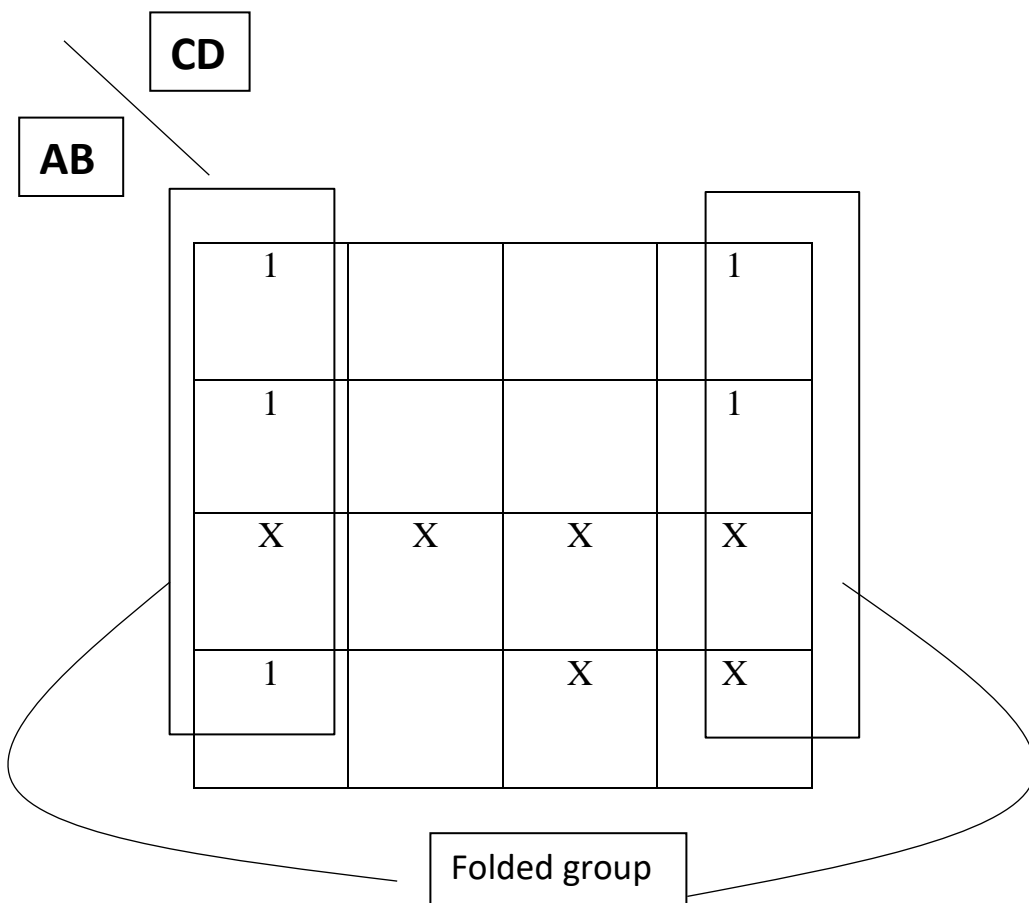

$Z = D'$

c) Logic Diagram

20P-0101, Muhammad Sherjeel Akhtar

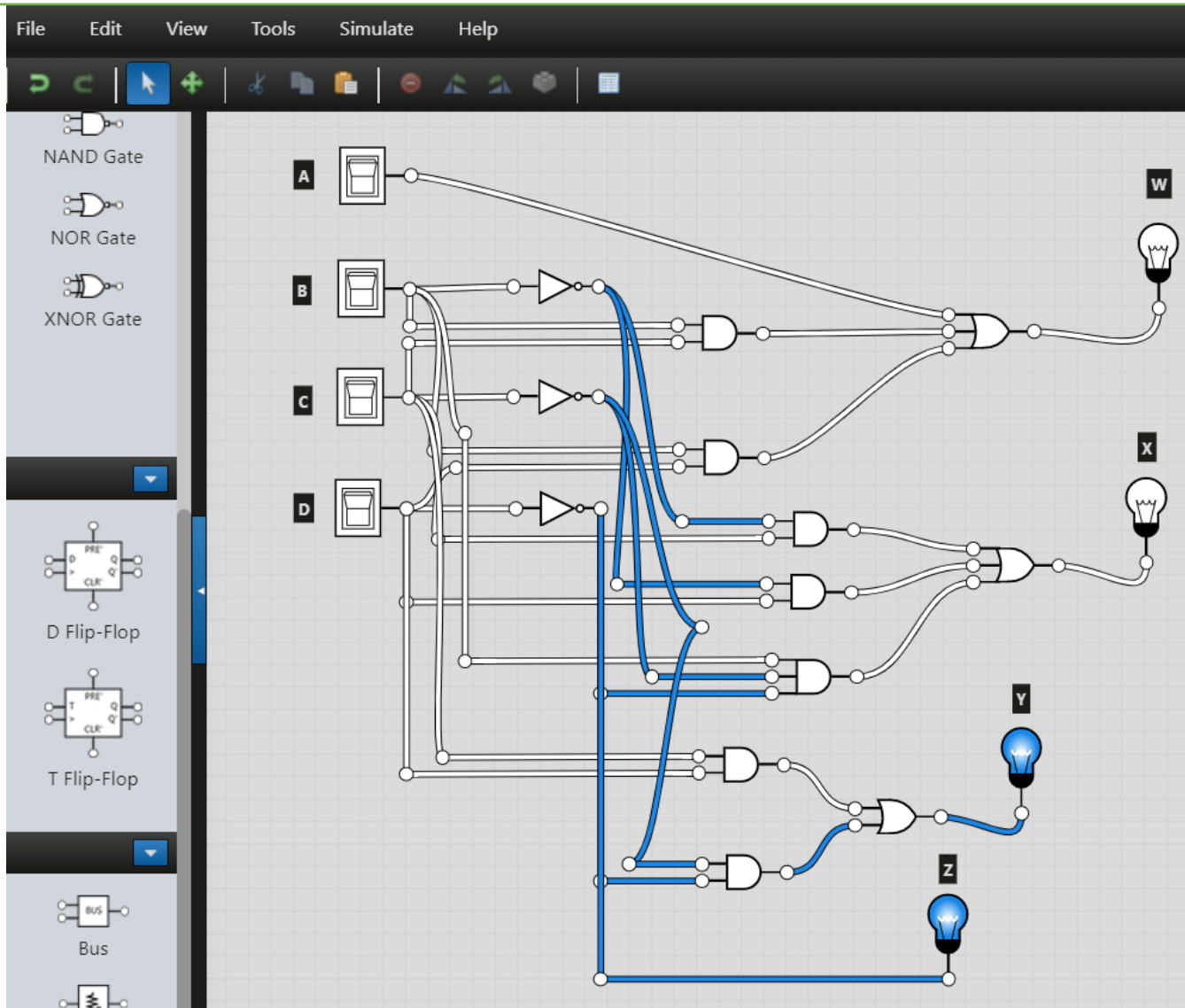

- d) Software Simulation (Show here your results for a few combinations to verify the circuit)

