

Lab 6

To Demonstrate the Working of Binary Subtractor

Note: You may draw all the logic diagrams with hand and paste the pictures here or on logicly software with your name, roll number & section mentioned in your workspace. Make sure that all of your connections are clearly visible and distinguishable.

Tasks

1. Construct a logic circuit for half and full subtractor with the help of truth table/Boolean expression. Also write the Boolean expression for output(s).

Half Subtractor

a) Truth Table

<u>X</u>	<u>Y</u>	<u>Difference</u>	<u>Borrow-out</u>
<u>0</u>	<u>0</u>	<u>0</u>	<u>0</u>
<u>0</u>	<u>1</u>	<u>1</u>	<u>1</u>
<u>1</u>	<u>0</u>	<u>1</u>	<u>0</u>
<u>1</u>	<u>1</u>	<u>0</u>	<u>0</u>


b) Boolean Expression (Simplified)

Difference: $X \oplus Y = X \text{ XOR } Y$

Borrow Out: $X' \cdot Y = \text{Not-X AND } Y$


c) Logic Diagram

→ Logic Diagram Of Half Subtractor:

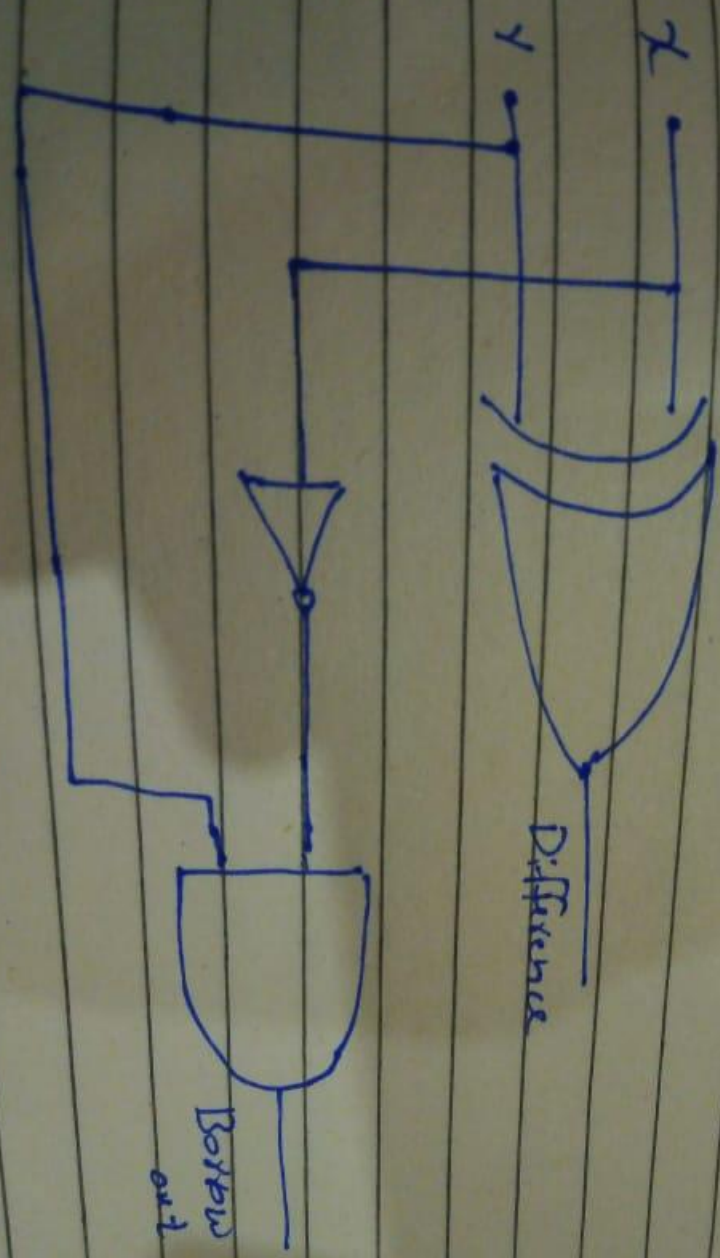


d) Software Simulation ([Show here your results for each combination that gives a high output](#))

1st High Output Simulation:

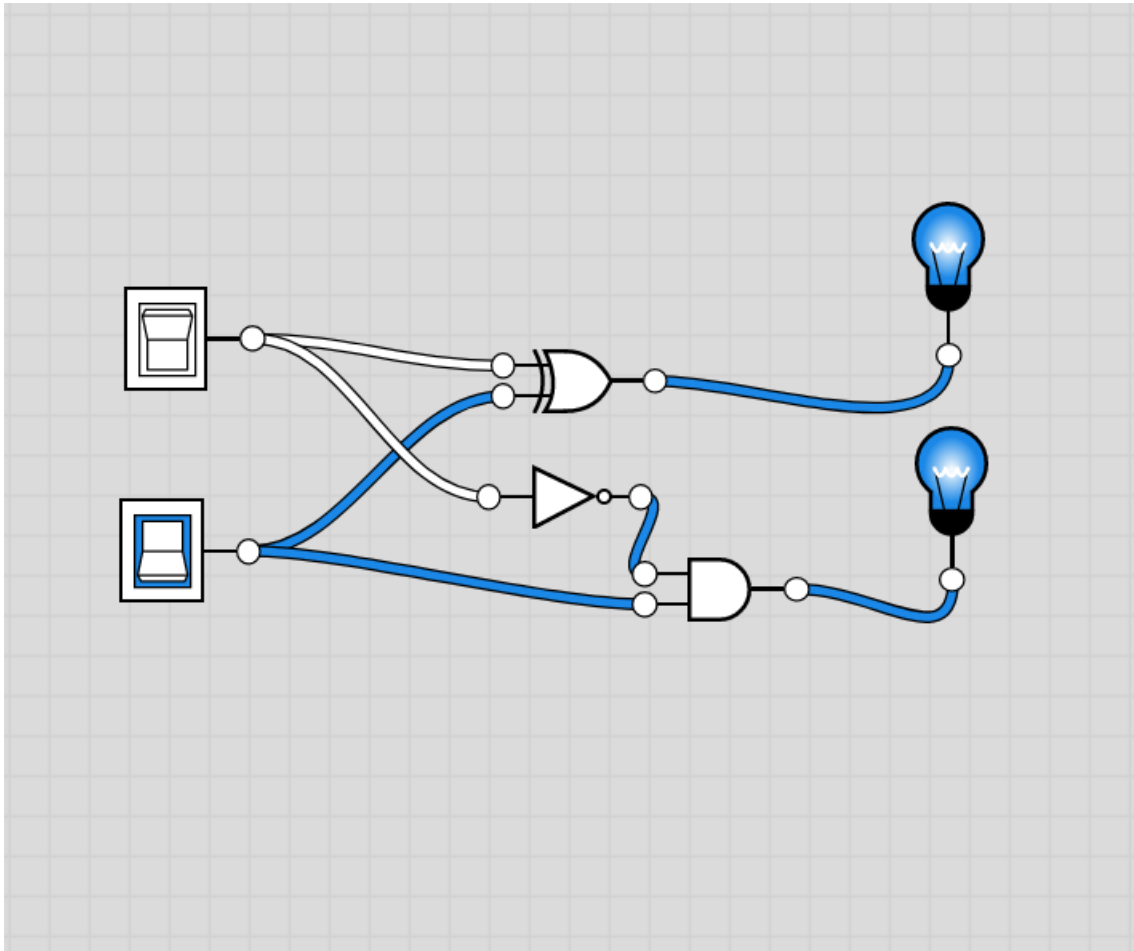

2nd High Output Simulation:

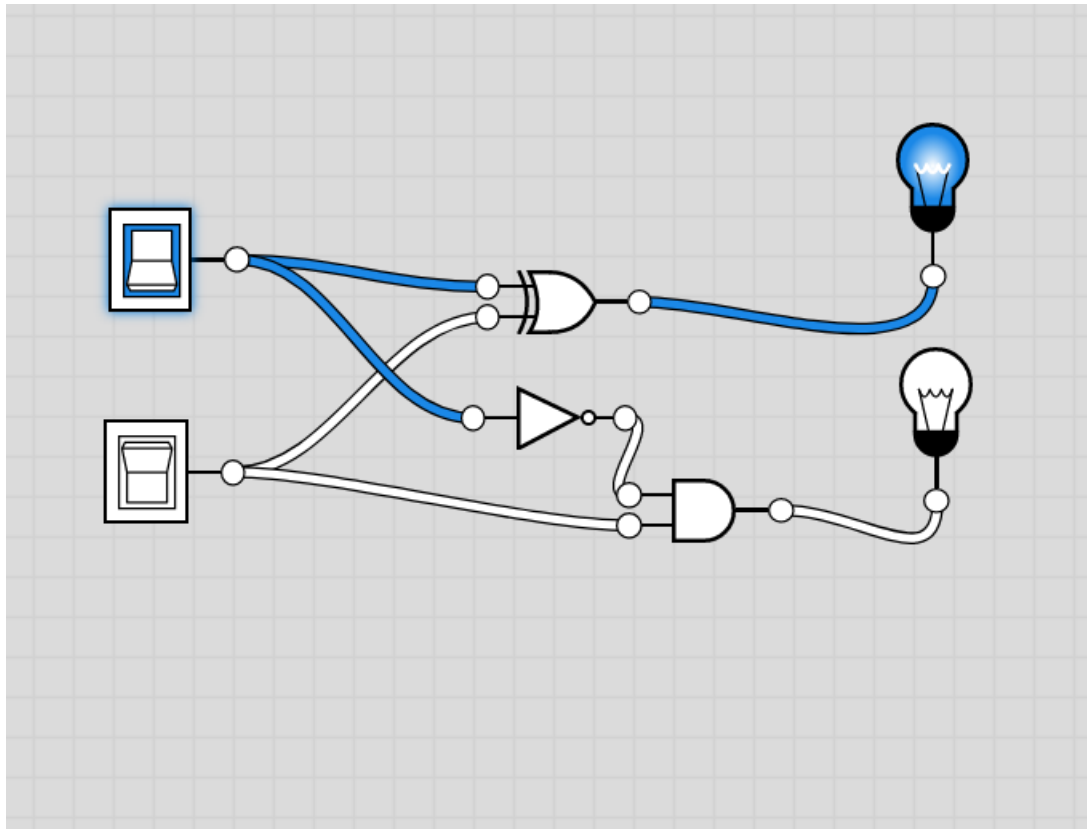

Full Subtractor

a) Truth Table

Bin	Y	X	Diff	Bout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	1
1	1	1	1	1

b) Boolean Expression (Simplified)

Difference: $(X \text{ XOR } Y) \text{ XOR } \text{Bin} = (X \oplus Y) \oplus \text{Bin}$

Borrow Out: $X' \text{ AND } Y \text{ OR } (X \text{ XOR } Y)' \text{ Bin} = (X \oplus Y)' \text{ Bin}$


c) Logic Diagram

→ Logic Diagram Of Full Adder:




d) Software Simulation (Show here your results for each combination that gives a high output)


1st High Output:

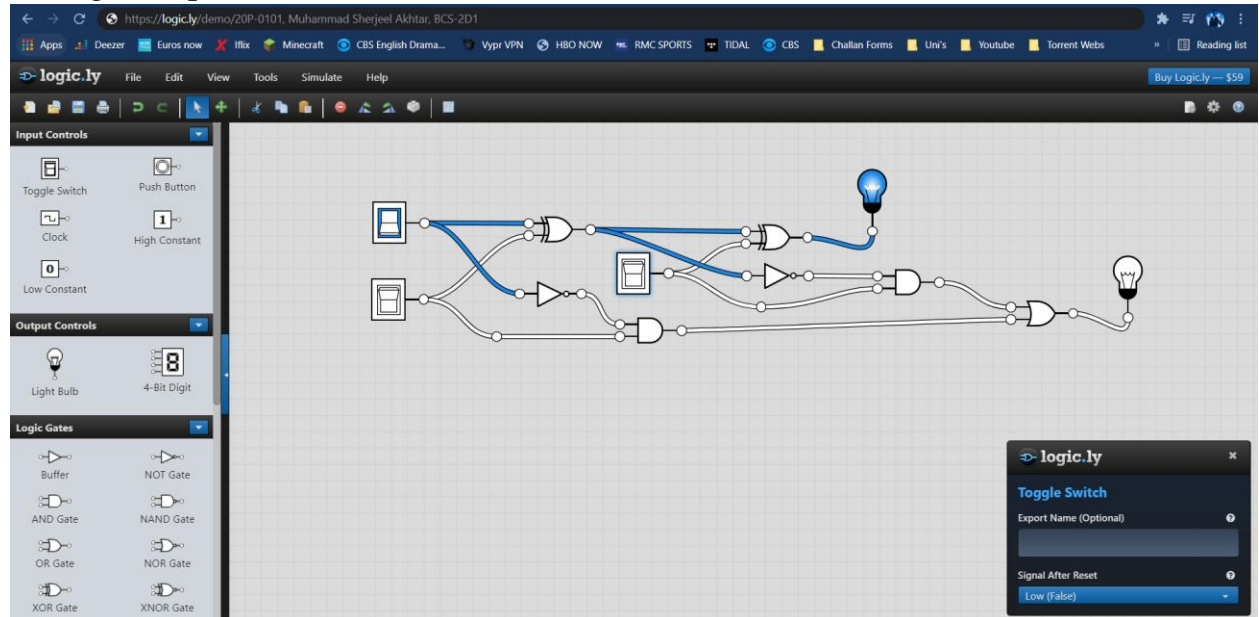


2nd High Output:

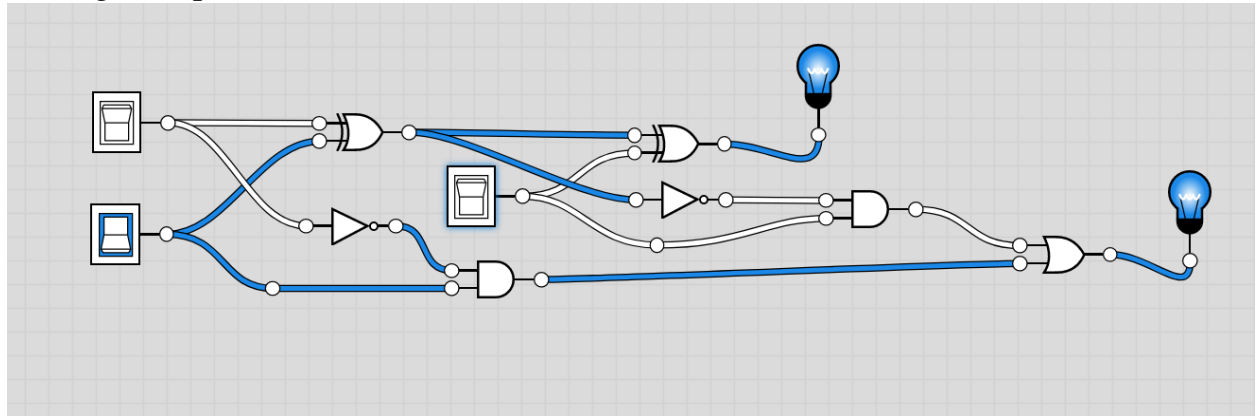

3rd High Output:

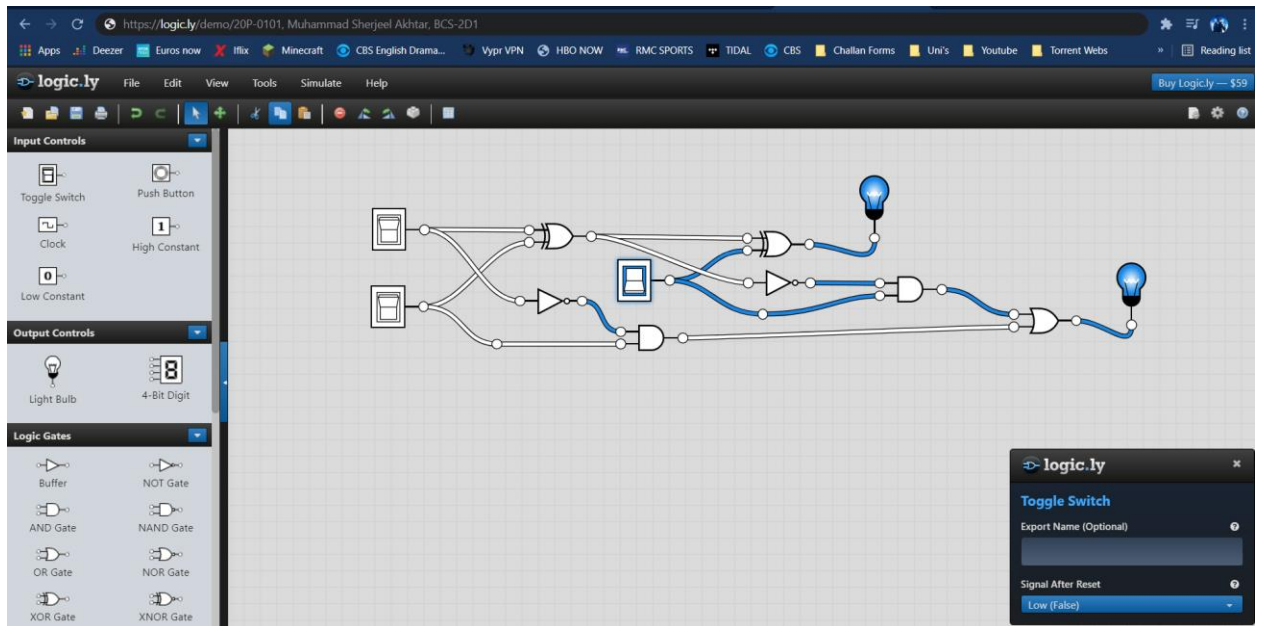

4th High Output:

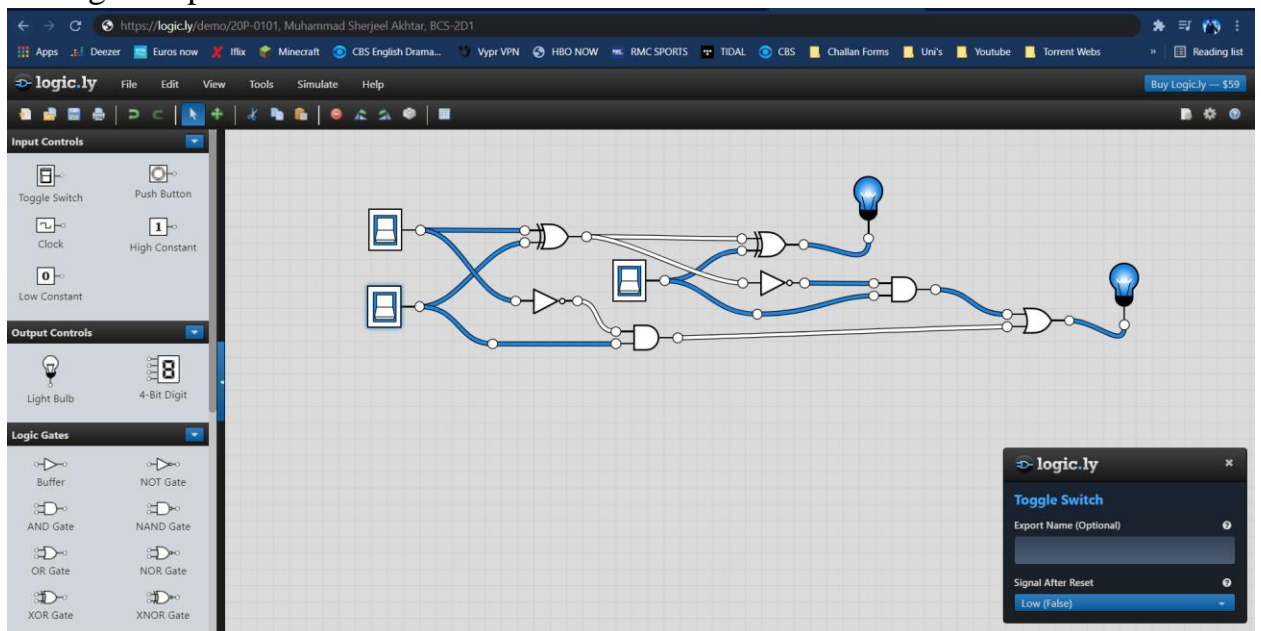

2. A full subtractor can be implemented using 2-half subtractors.


Demonstrate the logic diagram for the said circuit. Simulate your circuit for the verification of results.

a) Logic Diagram of Full Subtractor using 2-Half Subtractor




b) Software Simulation (Show here your results for each combination that gives a high output)


1st High Output:

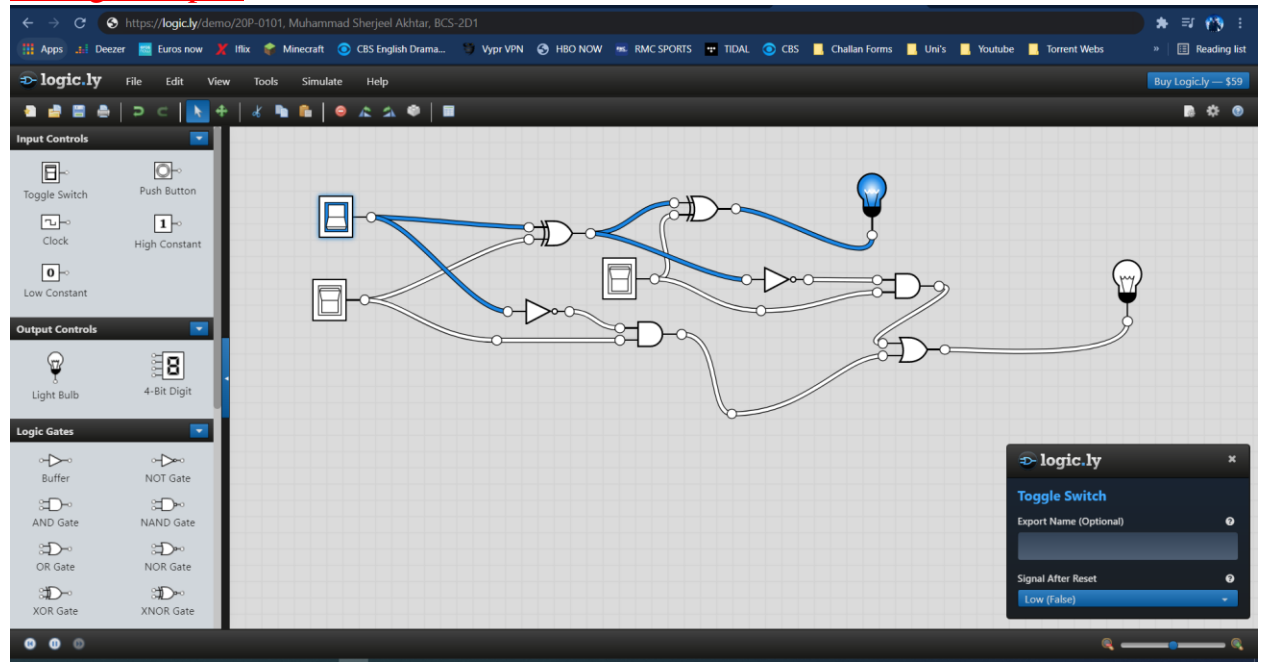

2nd High Output:

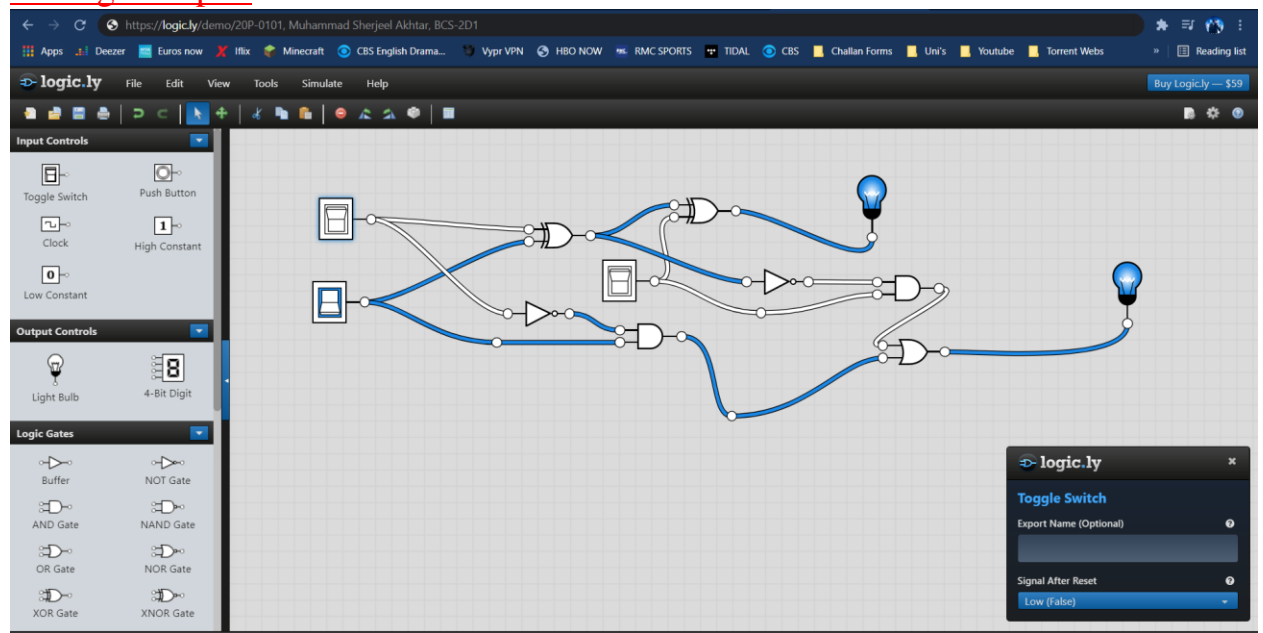

3rd high Output:

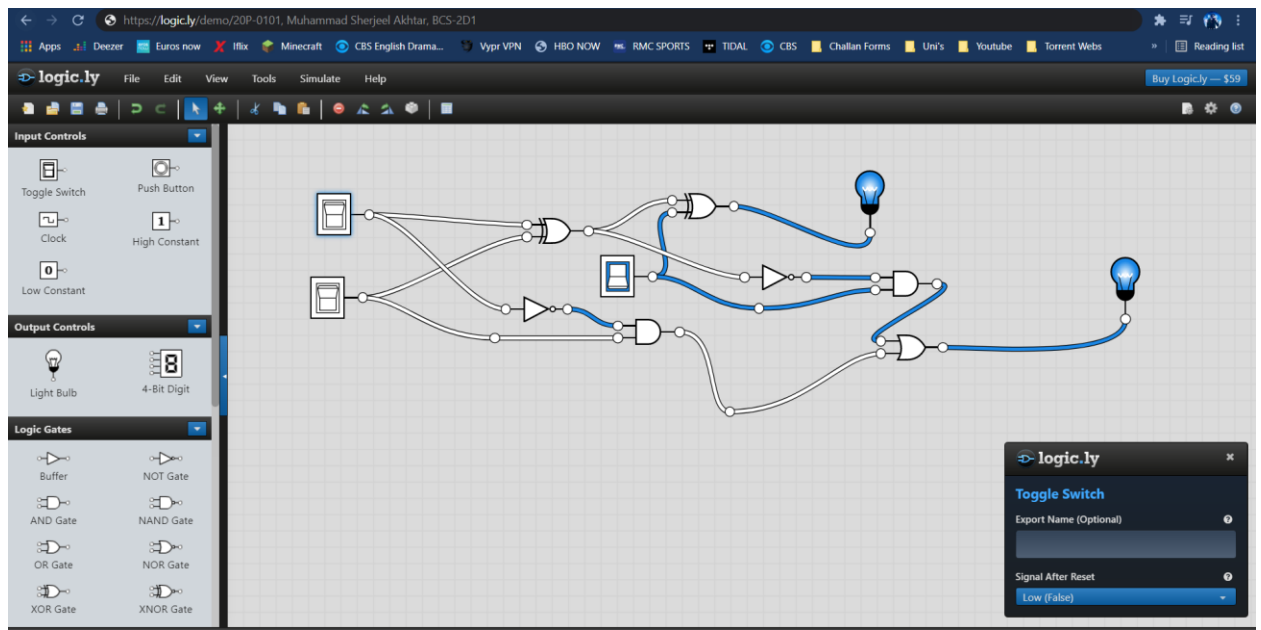

4th High Output:

